

PHEV – Plug-In Hybrid Electric Vehicle Charger

Advisors:

Dr. Woonki Na

Dr. Brian Huggins

Renee Kohl

Peter Burrmann

Matthew Daly

Why the electric car?

- Reduce our foreign oil dependence
- Reduce carbon emissions




Outline

- Functional Description
- Progression of Project
 - Implementation/Construction
 - Testing
- Results

Project Summary

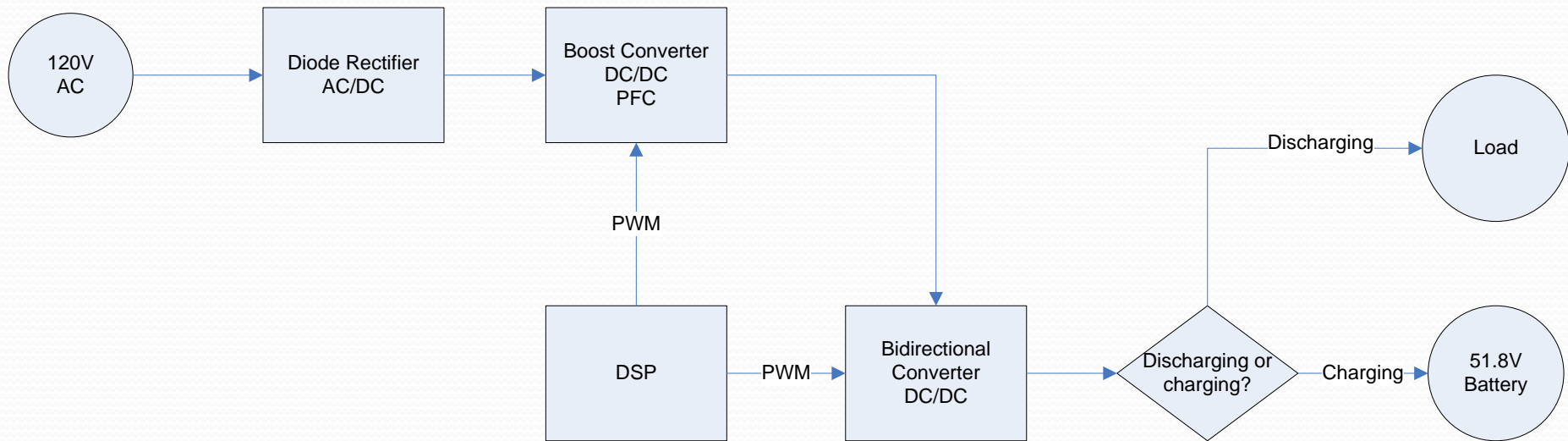
- Convert 120 volt AC grid power to the required 51.8[V] DC value to efficiently charge an electric vehicle battery
- Discharge battery via Bi-directional converter into a variable load



Project Goals

- Create a PHEV charging system capable of outputting up to 1k[W] of power for the operation of a variable load.
- Implement a control system using a DSP for the purpose of driving MOSFET gates
- Efficiently Charge a Li-Ion battery using our power electronics system



Diode Rectifier

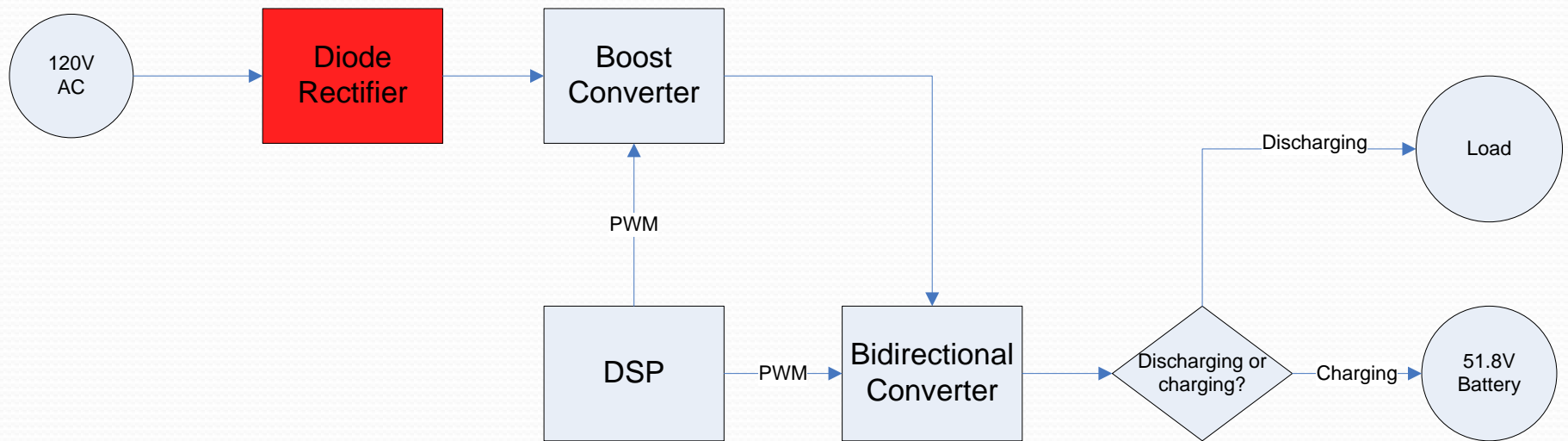

Functional Description


Diode Rectifier

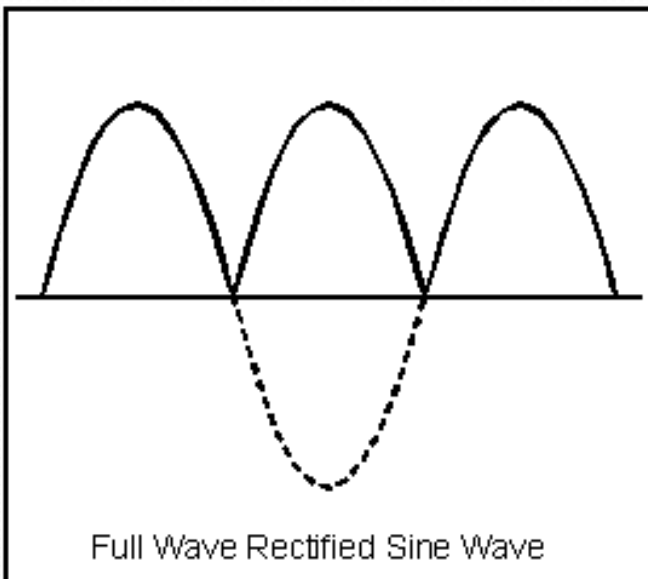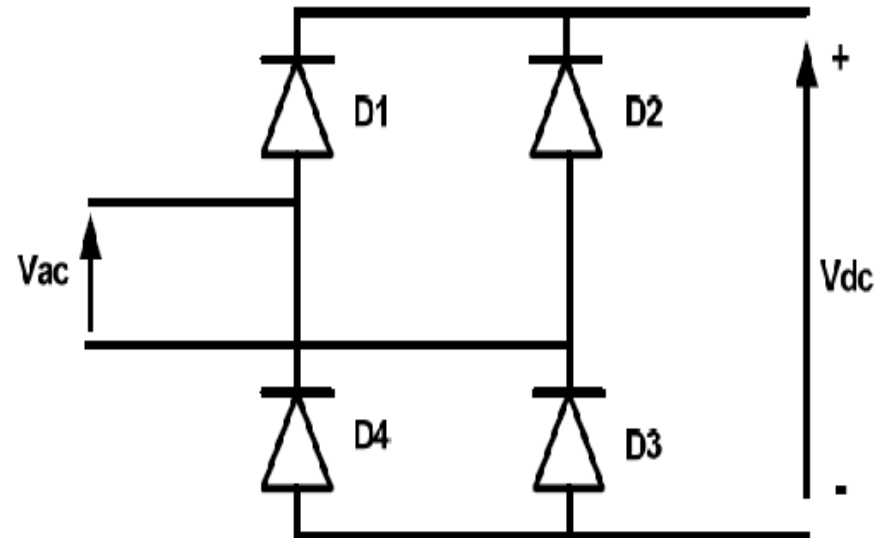- Rectifies 120 [V_{rms}] AC grid power
- Precedes Power Factor Correction




Functional Description

Diode Rectifier

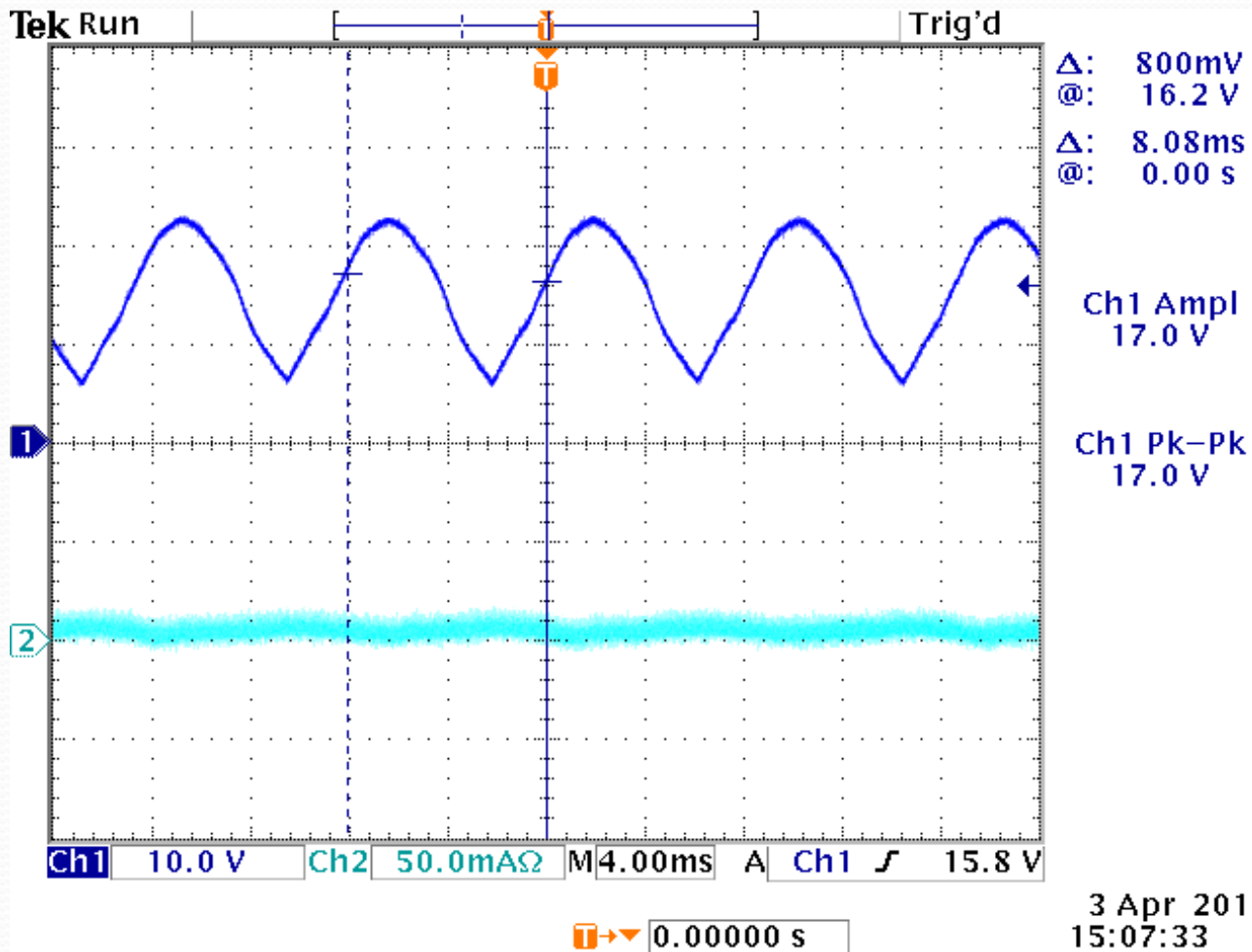


Power Factor Correction

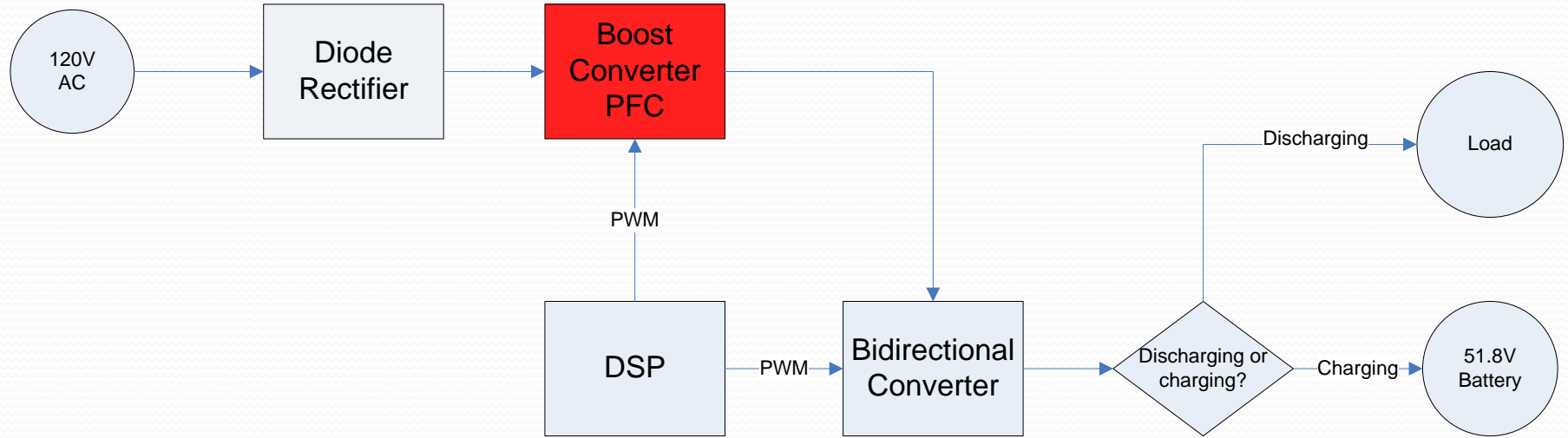


Power Factor Correction

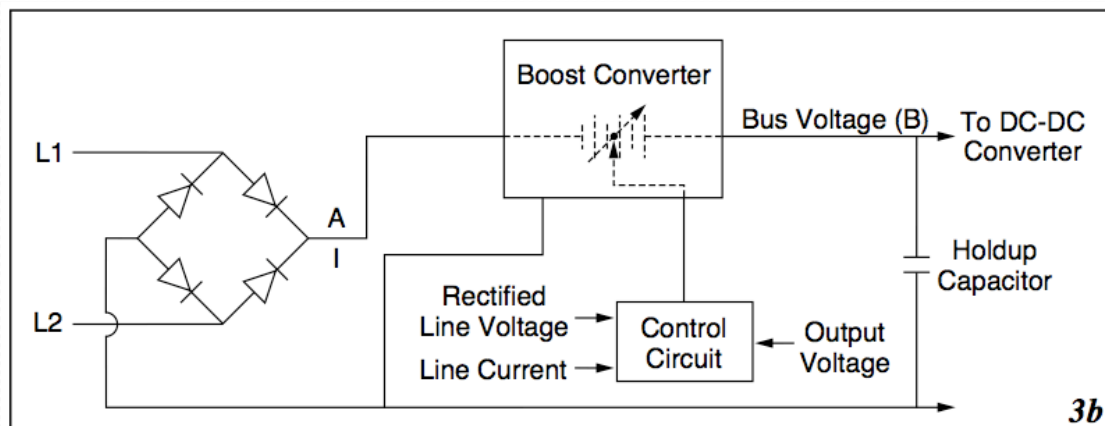- Power Factor
 - Dimensionless number from 0-1
 - Ratio of real to apparent power
 - 1 is in unity (ideal)
- Passive power factor correction- Capacitor, Inductor
- Active power factor correction- Boost Converter




Implementation

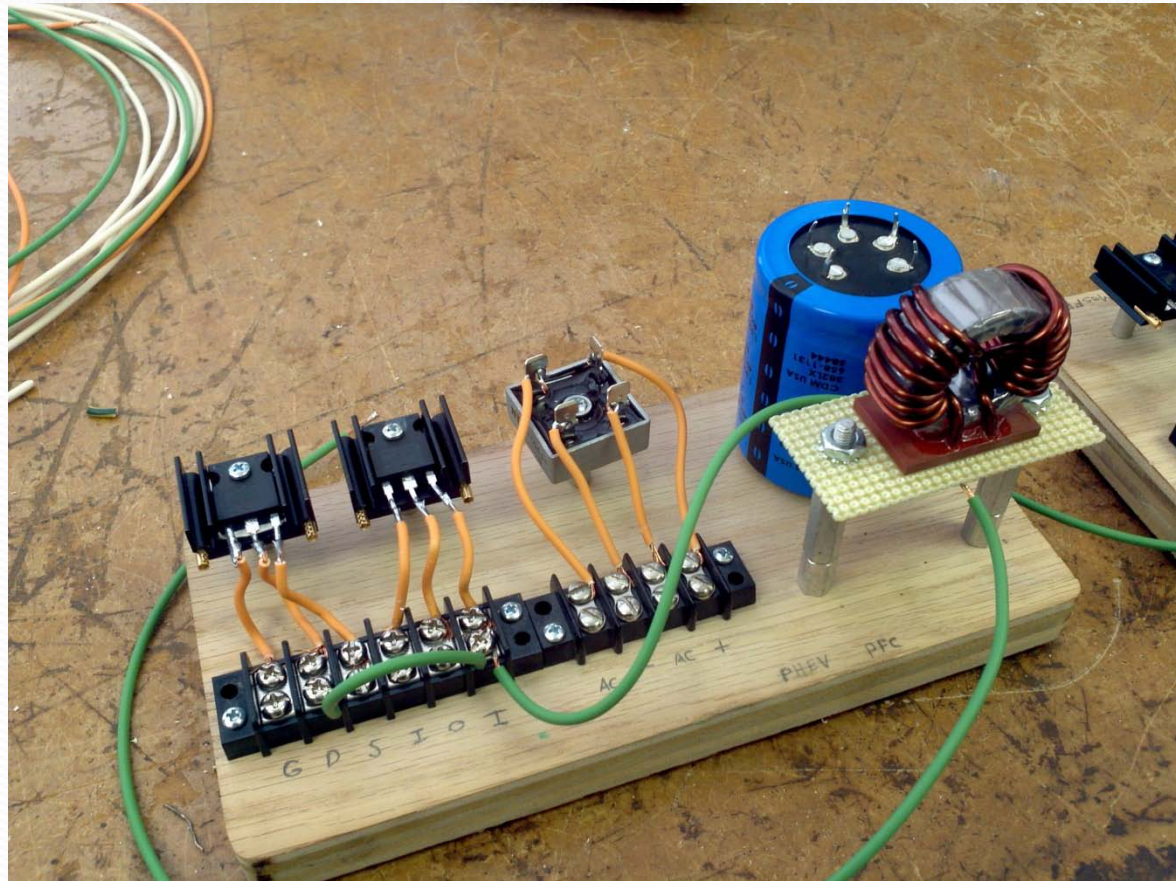Diode Rectifier / Power Factor Correction




Bi-Directional Converter

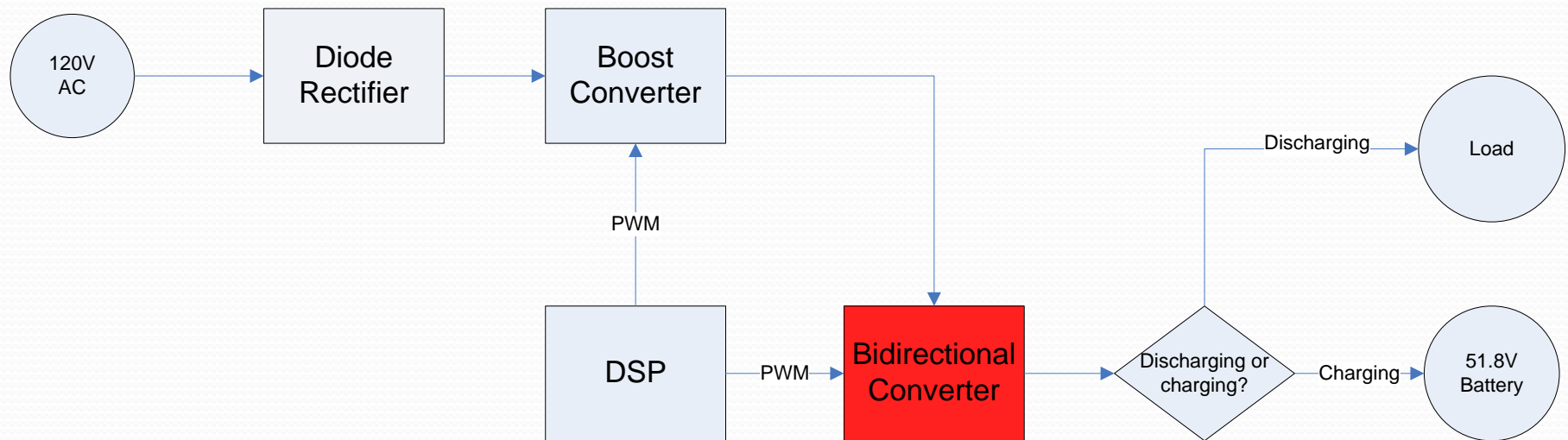

Functional Description


Bi-directional Converter

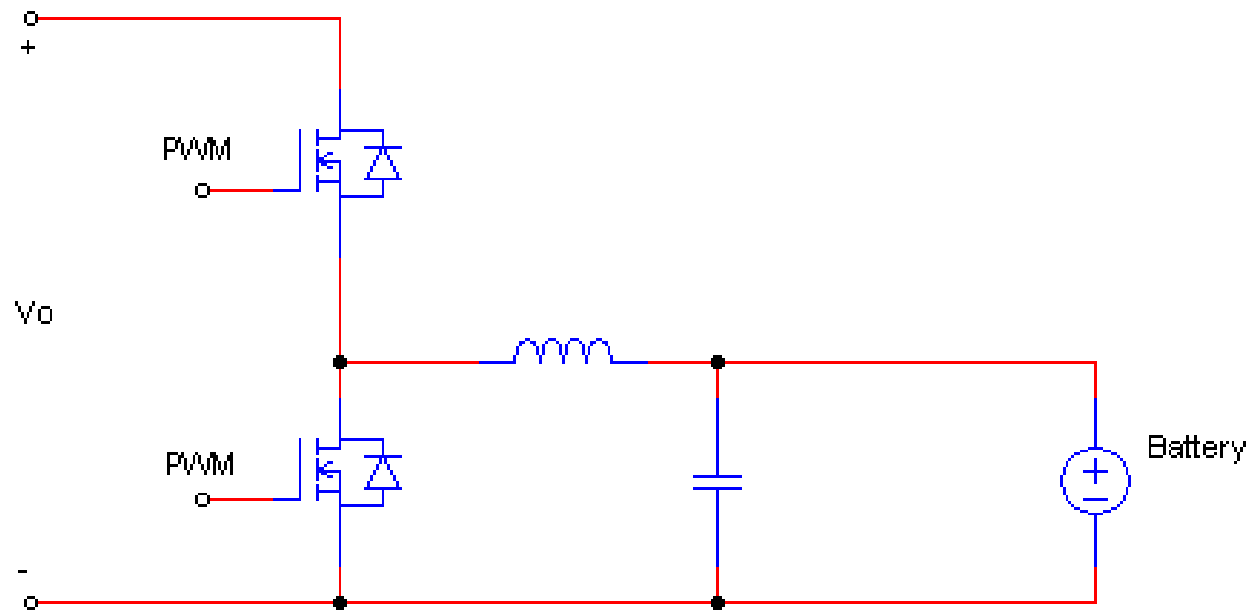- To be used in place of the individual Buck and Boost converters' architecture
- Requires more detailed control system



Implementation


Bi-Directional Converter

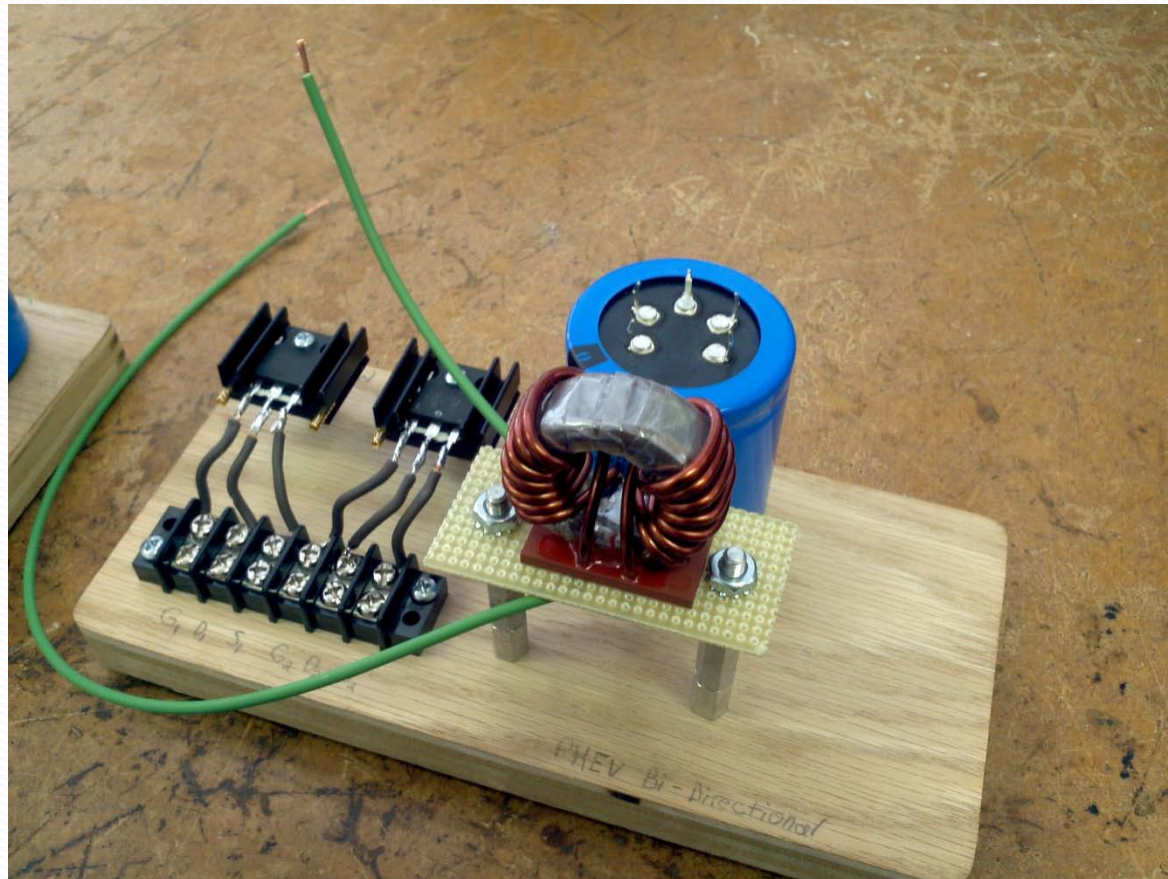


Functional Description

Buck Converter

- Drops input voltage based on MOSFET Duty cycle
- Half of the Bi-directional Converter

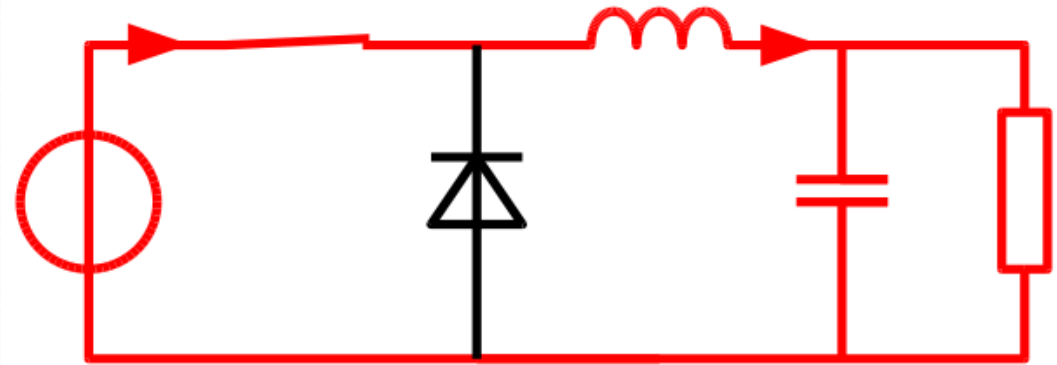

Stage 1

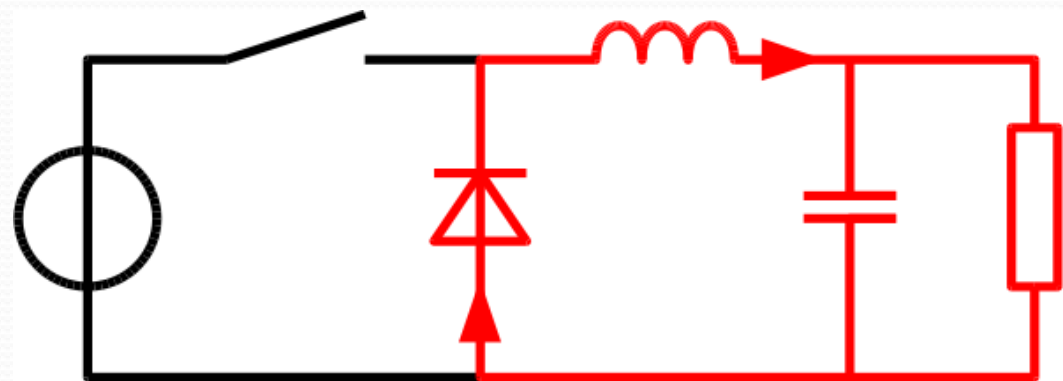


Stage 2


Functional Description

Boost Converter

- Boosts input voltage based on MOSFET duty cycle
- Part of Power Factor Correction
- Half of Bi-directional Converter

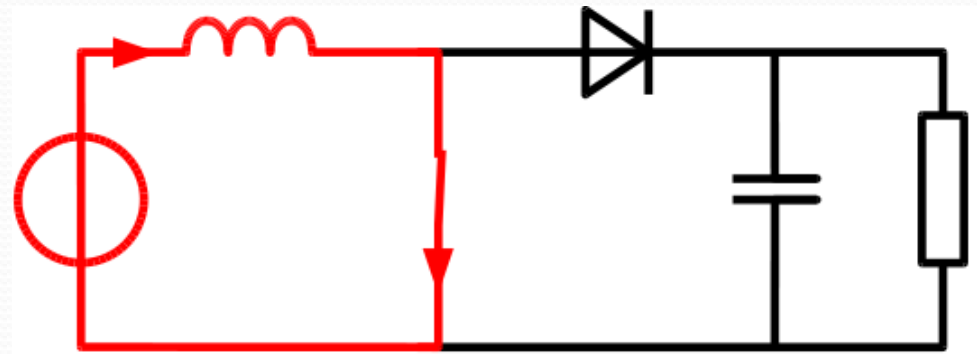


Stage 1

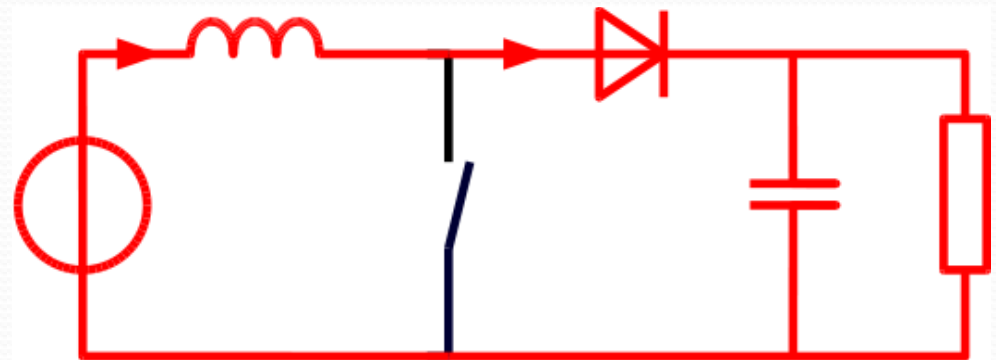

Stage 2

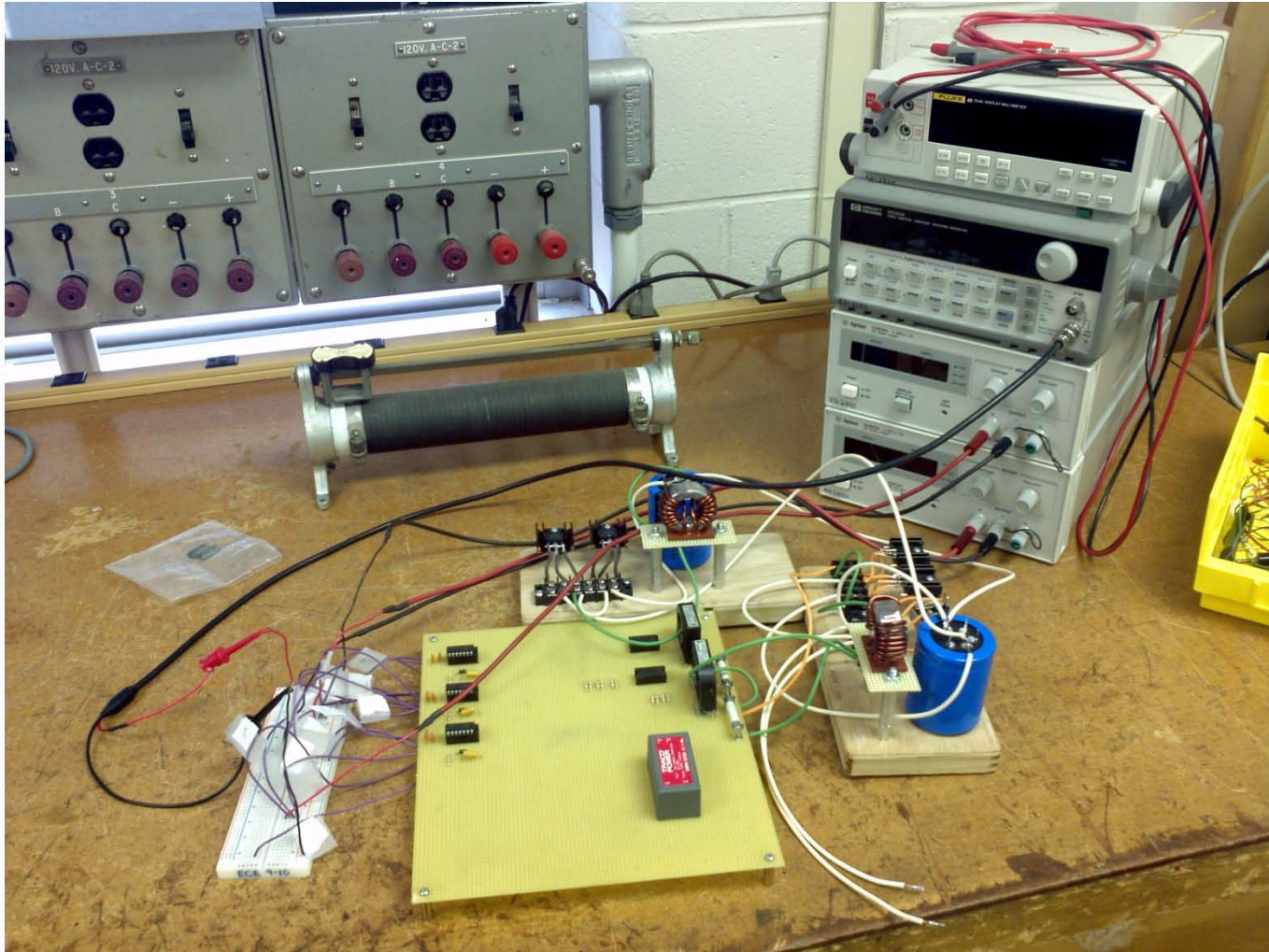
Implementation PFC and Bi-Directional Converter



Functional Description

Interfacing & Protection Circuitry

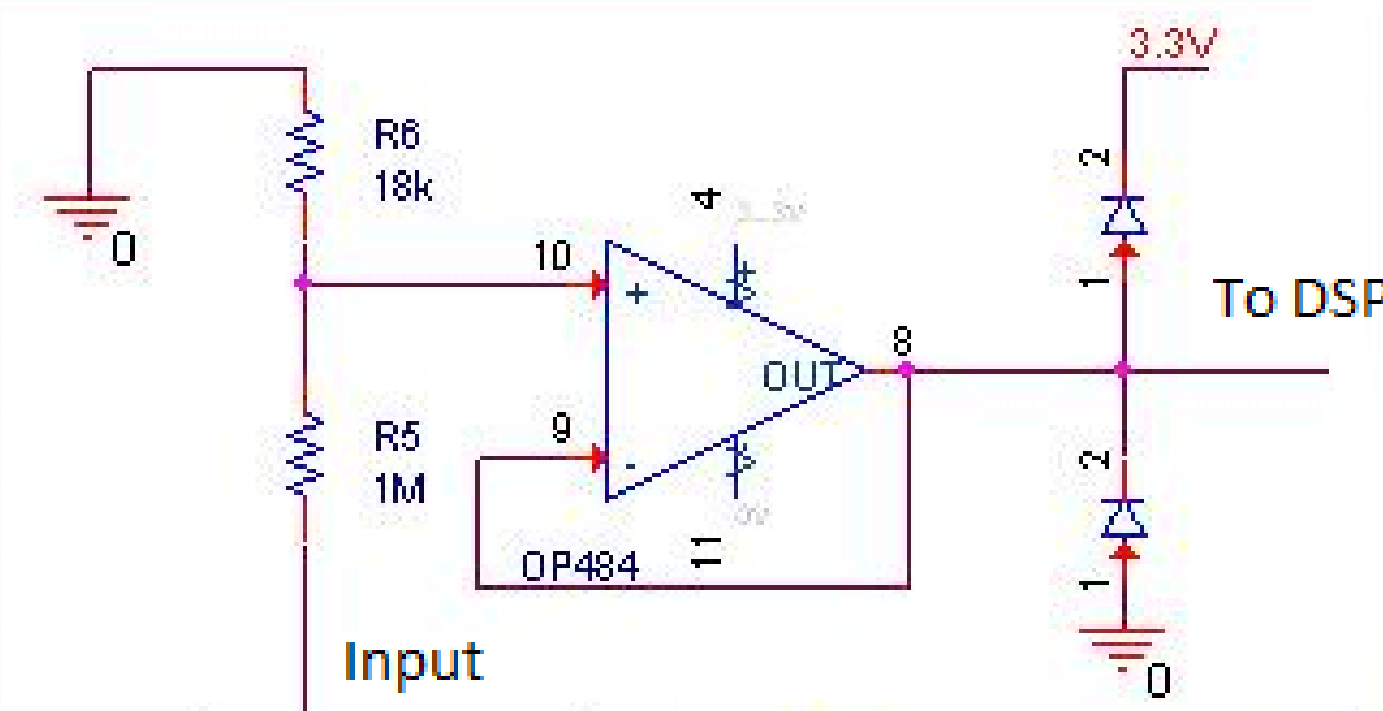
- To be used to sense voltage levels from various locations of the PHEV system, while providing isolation between the DSP and high voltage levels



Functional Description

Gate Driver

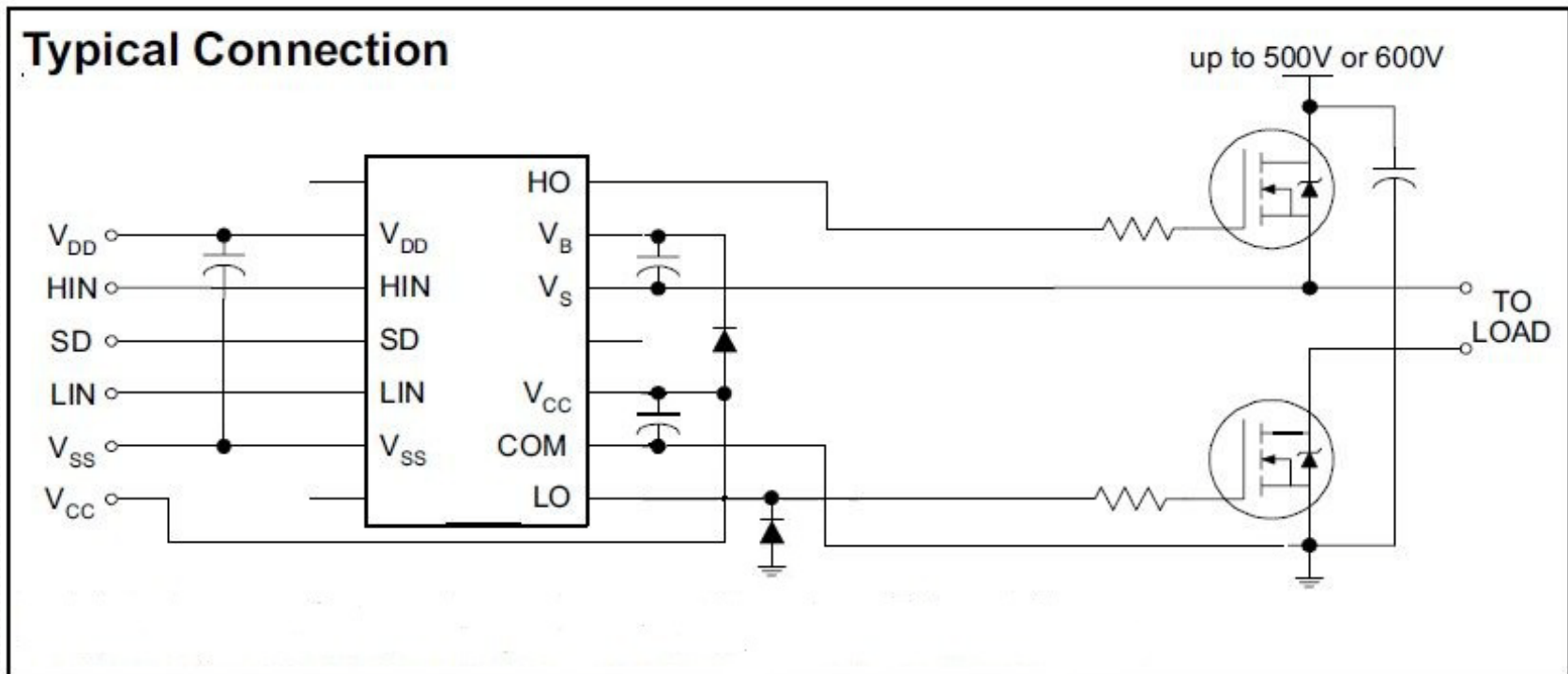- Receives PWM input from DSP to control switching of MOSFETs
- Provides enough power to drive the converter's MOSFETs



Functional Description

Gate Driver

Bootstrap Capacitor


$$C \geq \frac{2 \left[2Q_g + \frac{I_{qbs(max)}}{f} + Q_{ls} + \frac{I_{cbs(leak)}}{f} \right]}{V_{cc} - V_f - V_{LS} - V_{Min}}$$

$$I_g = \frac{Q_g}{T_s}$$

$$R_g = \frac{V_g}{I_g}$$

Q_g	= Gate Charge
f	= Frequency of Operation
$I_{qbs(max)}$	= Maximum V_{bs} Quiescent Current
Q_{ls}	= Level Shift Charge (5nC)
$I_{cbs(leak)}$	= Leakage Current
V_{cc}	= Logic Section Voltage Source
V_f	= Forward Voltage Drop Across Bootstrap Diode
V_{LS}	= Voltage Drop Across Low- Side FET
V_{min}	= Minimum Voltage Between V_b and V_s

Battery

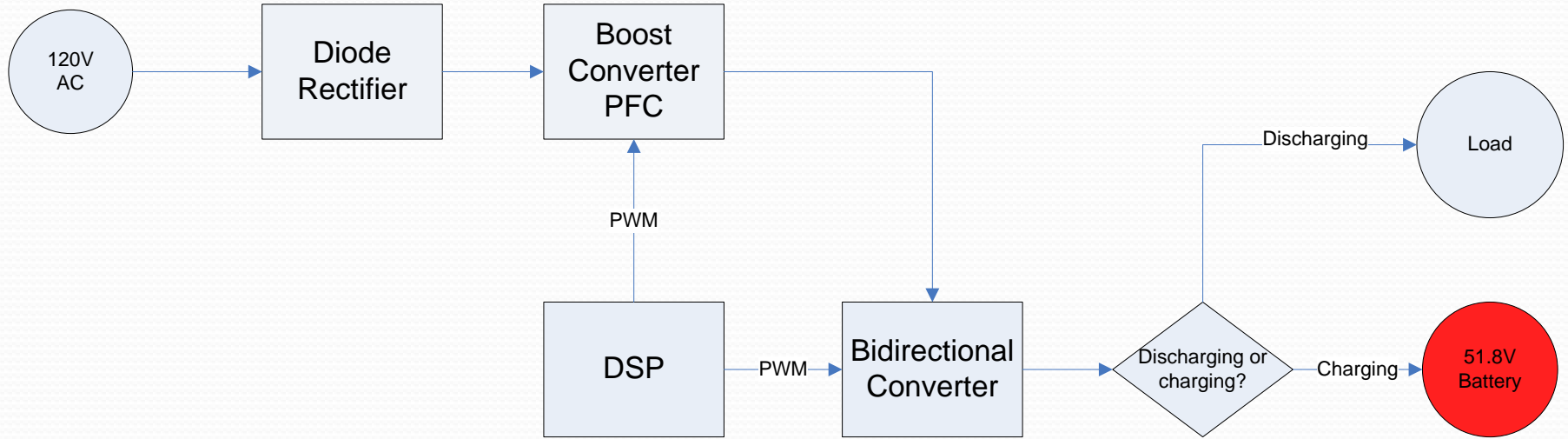


Functional Description

Battery

- Working Voltage=51.8[V]
- 14 Cell Polymer Li-Ion
- Capacity = 10Ah (518Wh)
- 40[A] Continuous Discharge Rate



Functional Description Battery

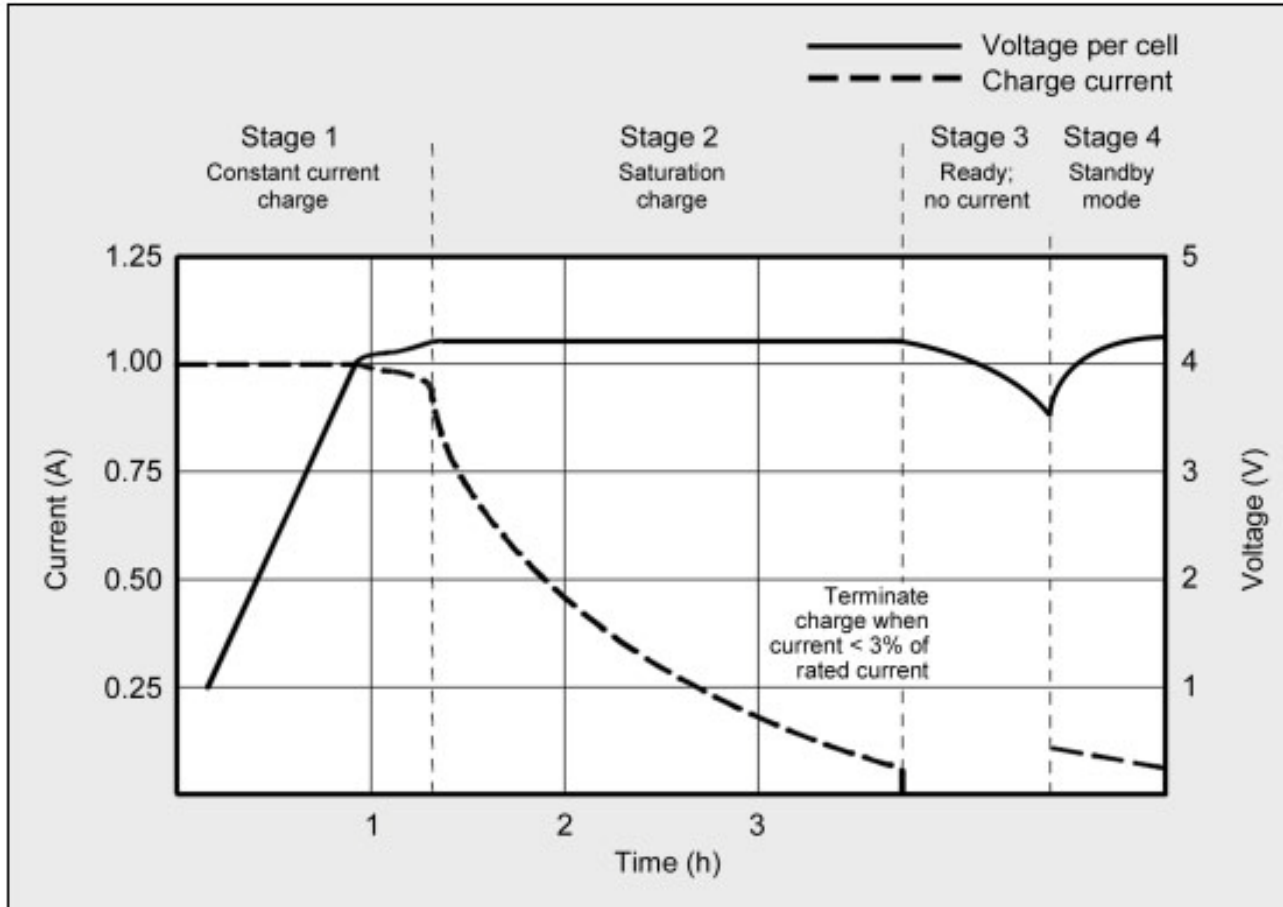

Stage 1
Voltage rises at
constant current

Stage 2
Voltage peaks,
current decreases

Stage 3
Charge
terminates

Stage 4
Occasional
topping charge

Implementation


Charging Method

- Stage 1: Charge Rate: 0.8C
 - Constant Current Method
- Stage 2: 58.8[V]
 - Constant Voltage Method
 - Terminate at 3% Rated Current
- No Trickle Charge
 - Reduces battery life

Implementation

Battery Resistance

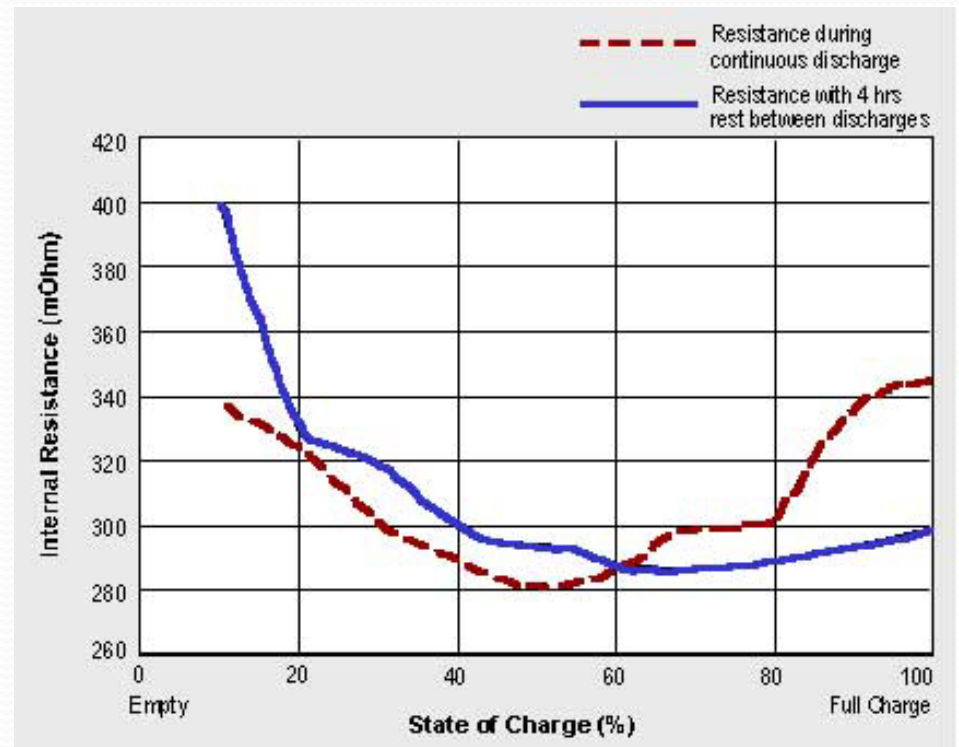
- Internal Resistance varies with State of Charge
- Actively Measure State of Charge
- Coulomb Counting
 - Requires Current Shunt



Implementation

Measuring Battery Resistance

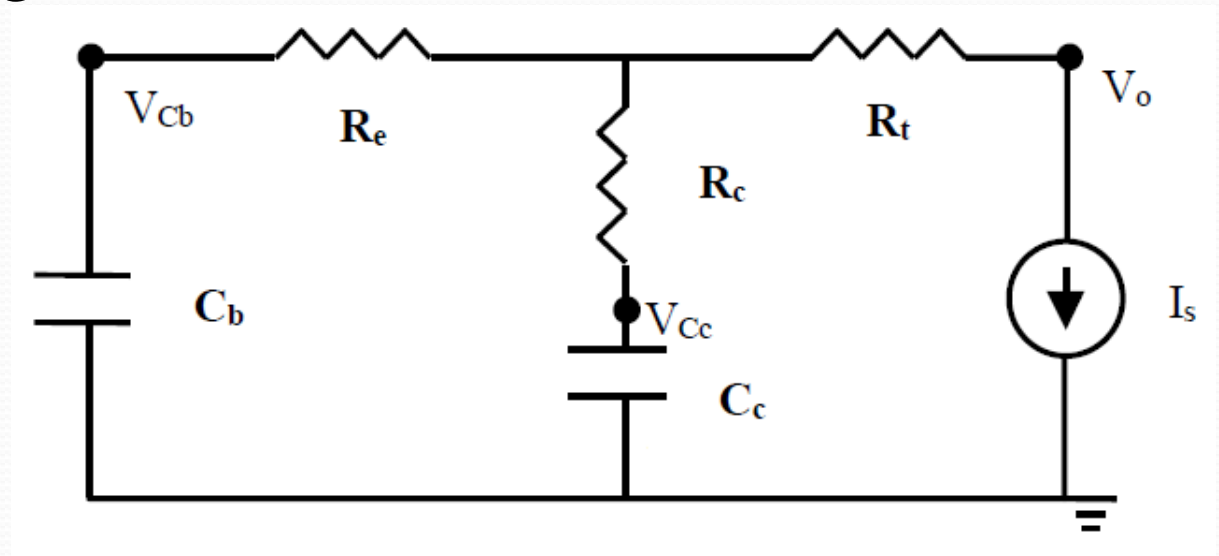- RC Battery Model
- Allows for Matlab simulation
- Resistance values are functions of SOC, T, and charge/discharge




Implementation

Measuring Battery Resistance

- Internal Resistance seen from pulse discharge
- $R_{\text{int}} = 108\text{m}[\Omega]$


$$R = \frac{V_{\text{oc}} - V_{\text{terminal}}}{I} = \frac{V_3 - V_2}{I}$$

Vr	56.530
R	10.910
V1	57.850
V2	57.160
V3	57.720
I	5.181
Rint	0.108

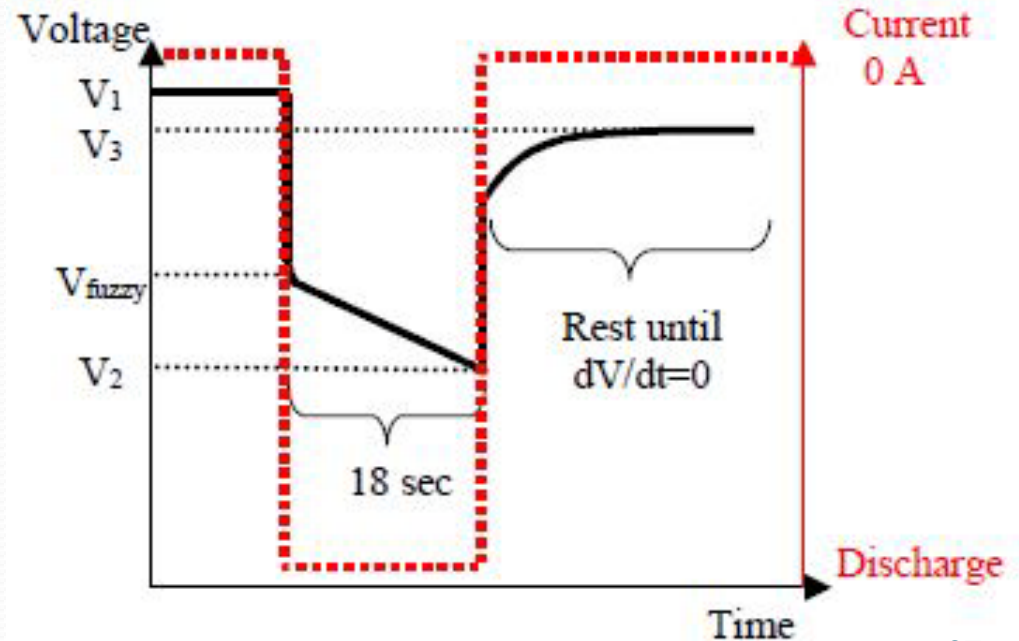


Implementation

Measuring Battery Resistance

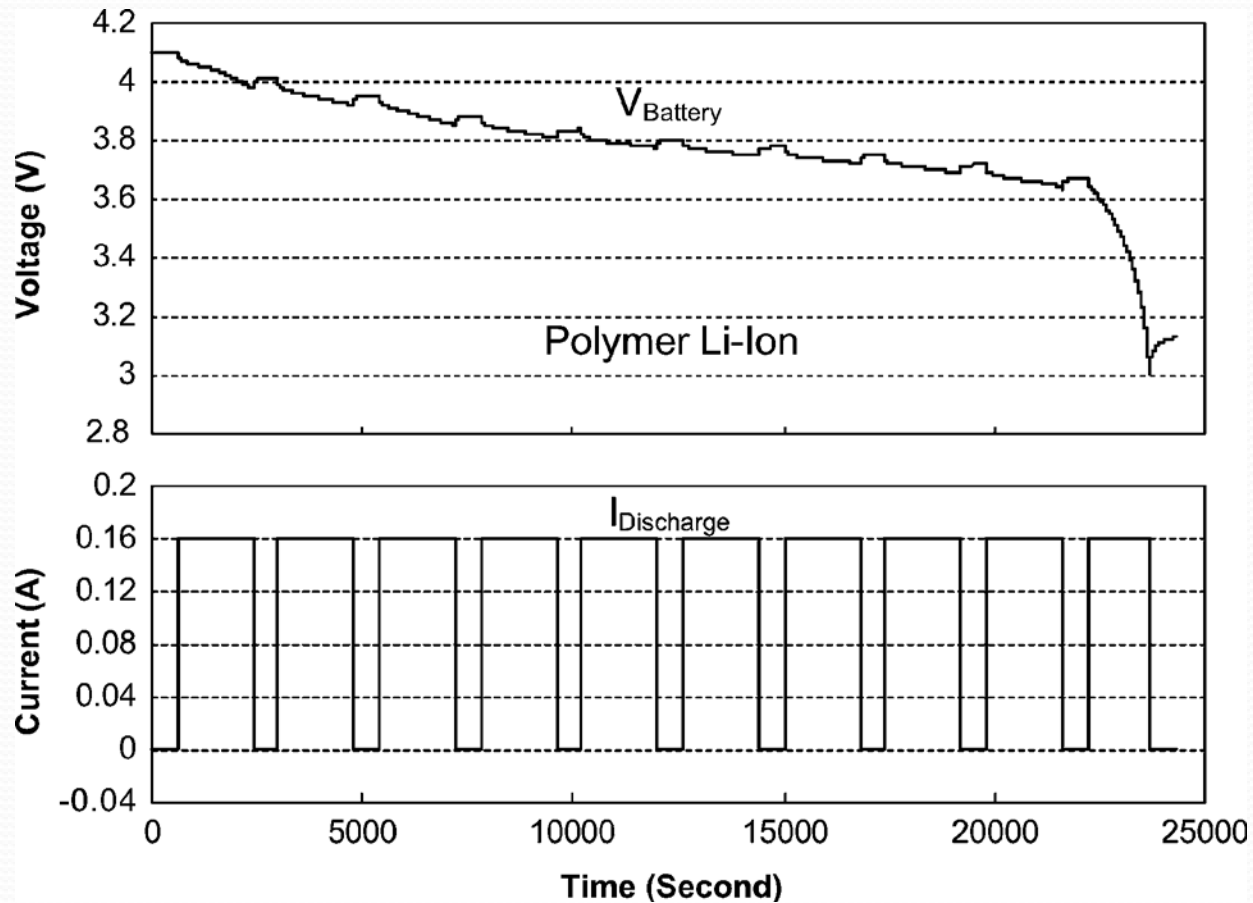


Bi-Directional Converter

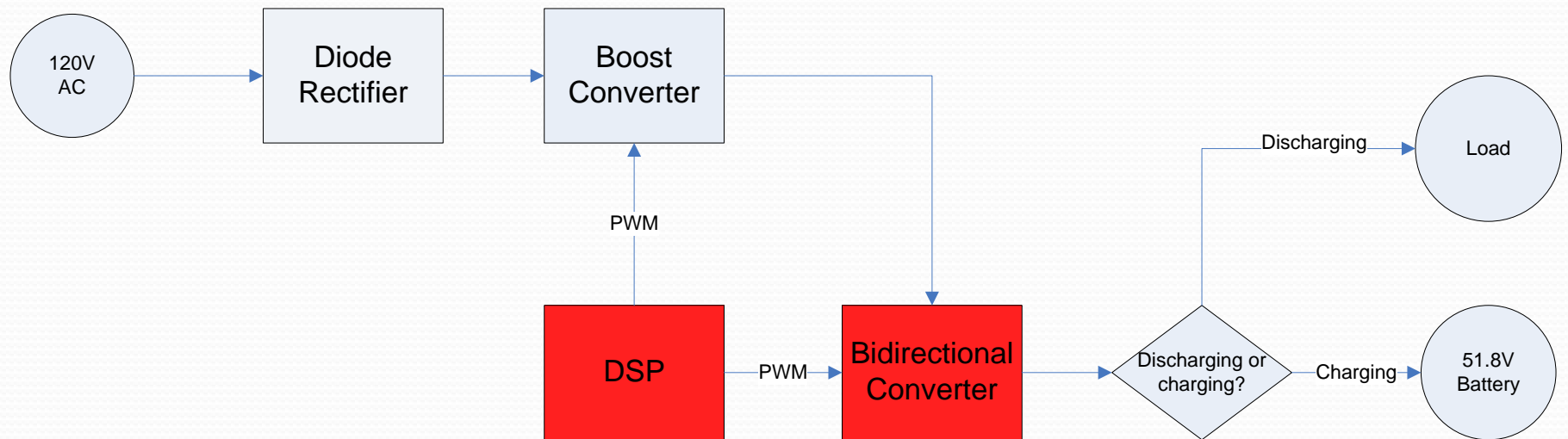


Schematics


- Buck Converter

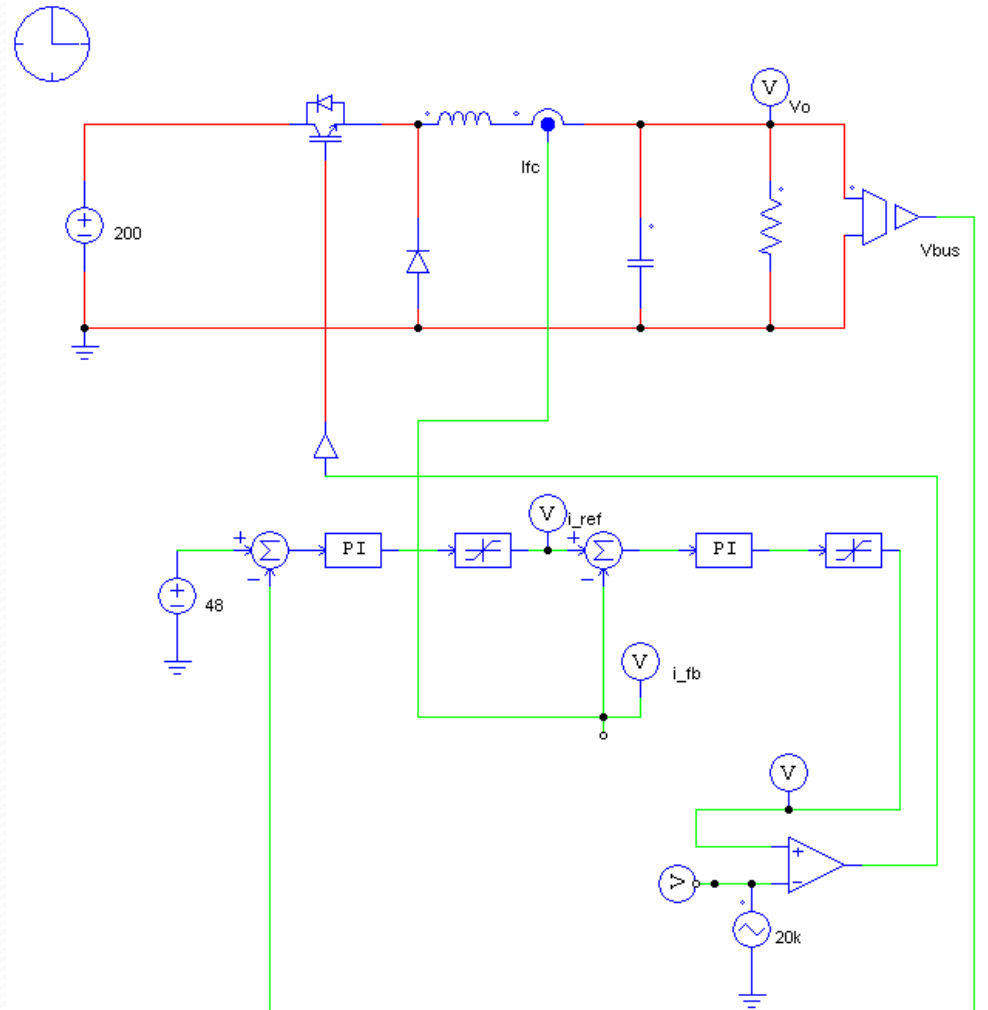


Calculating gains

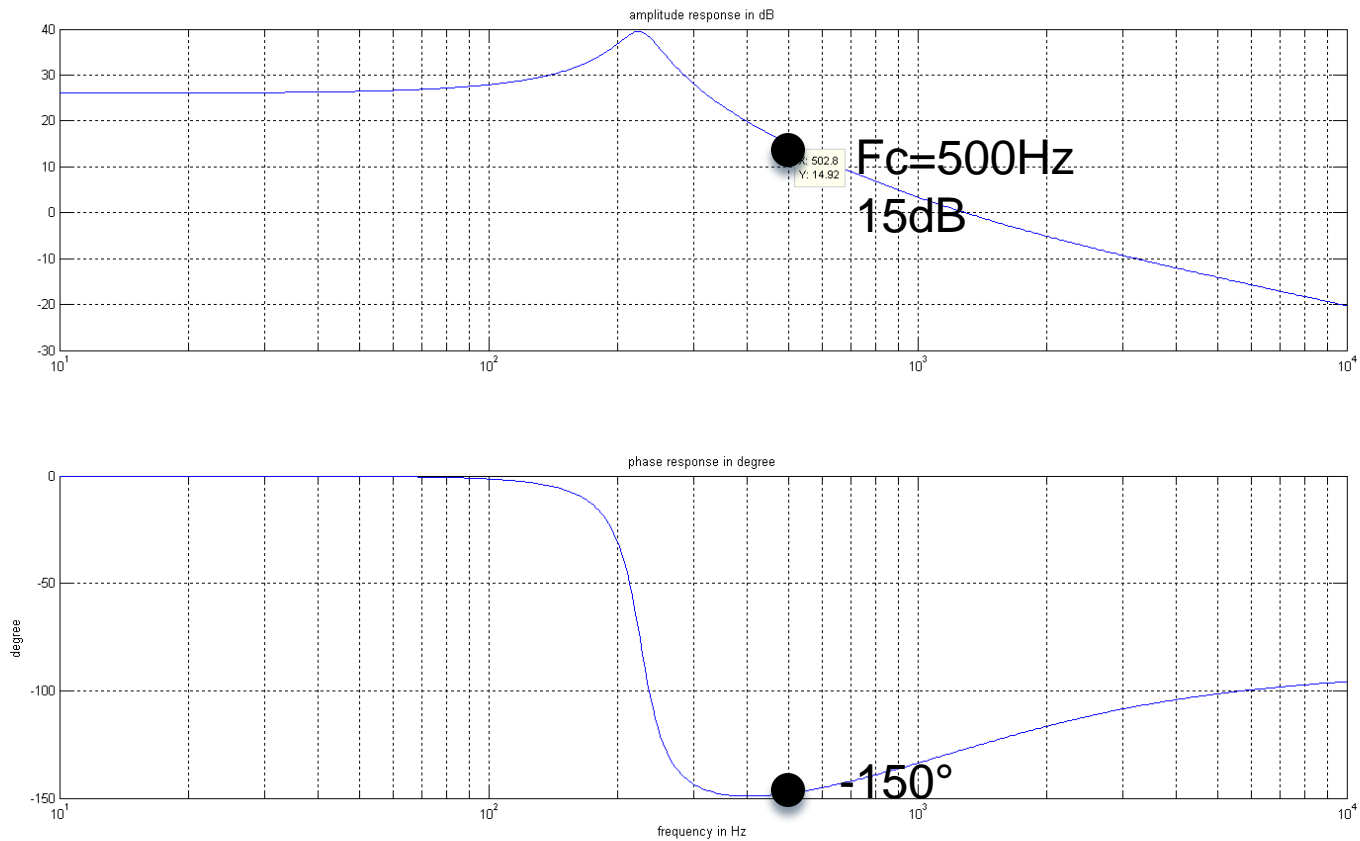





Psim output voltage

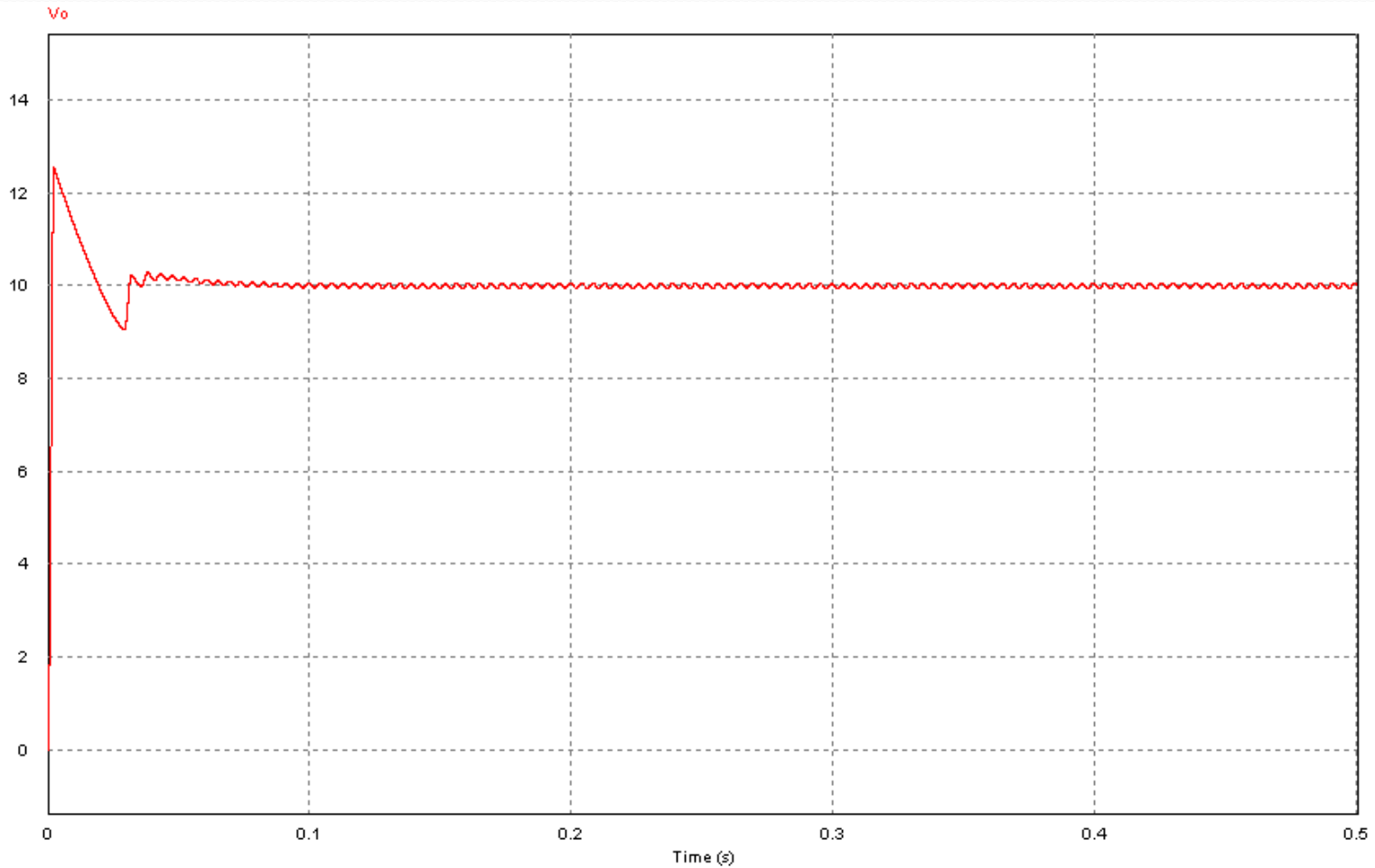

Buck Converter PI Control

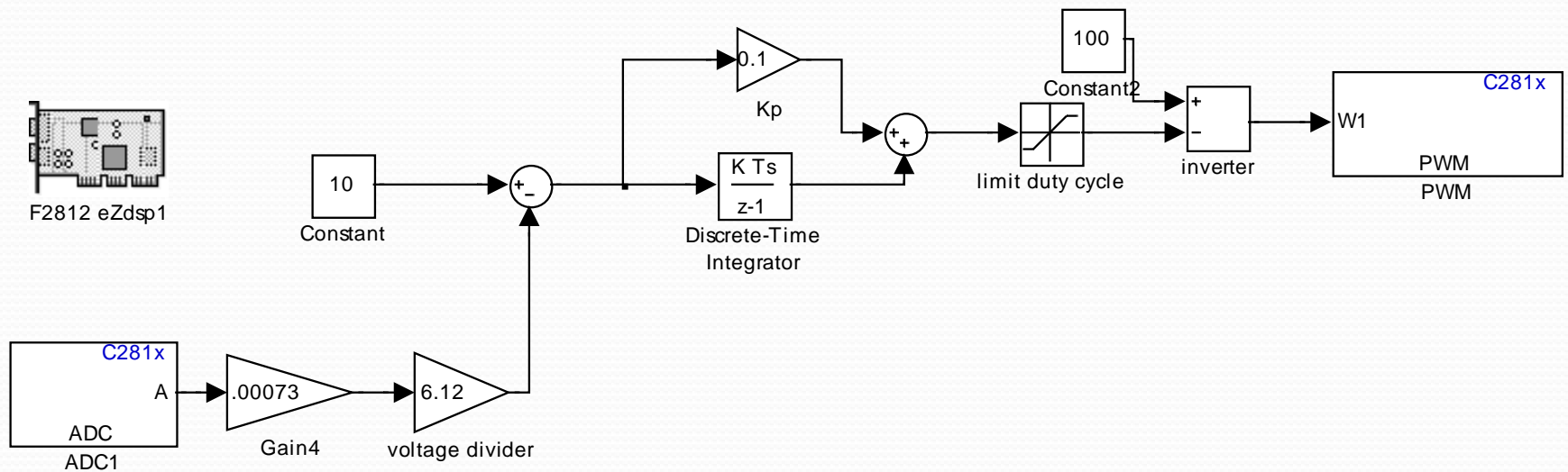


PI Control

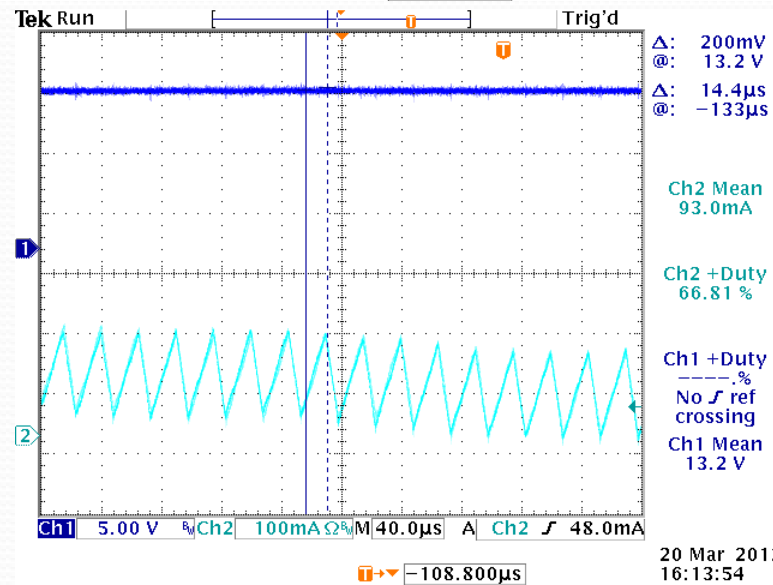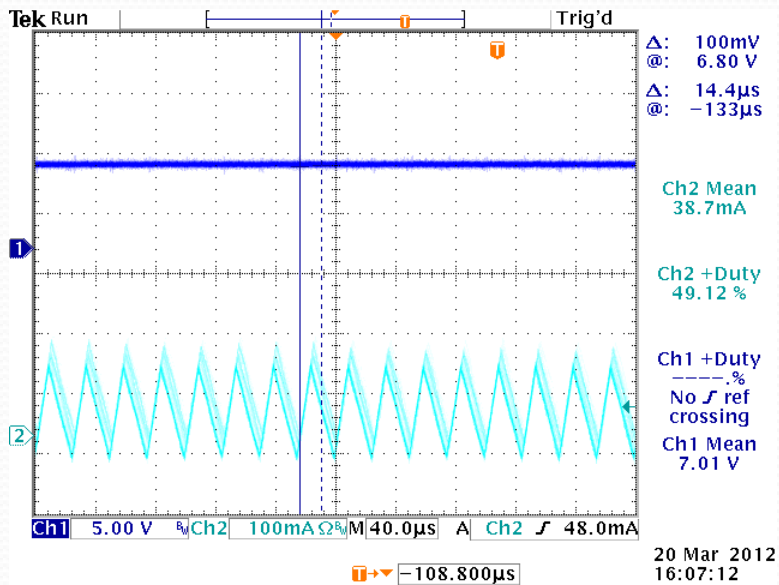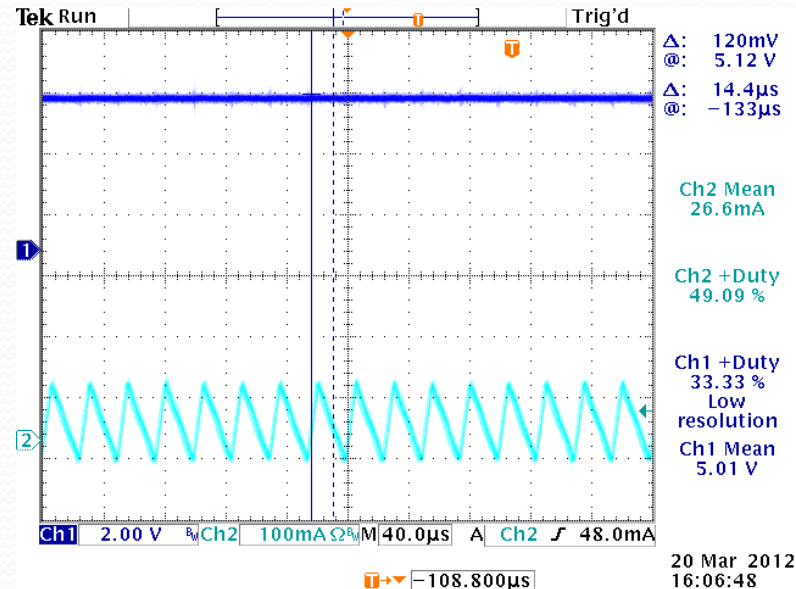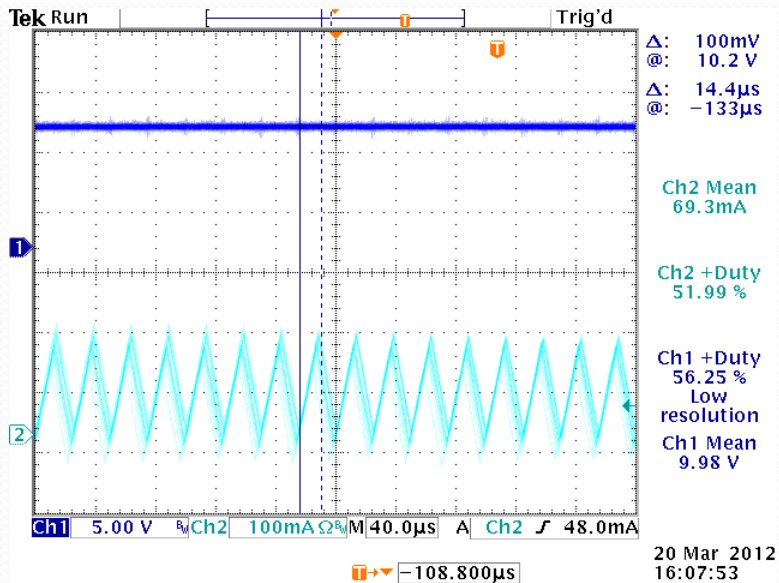


Schematics


- Boost Converter

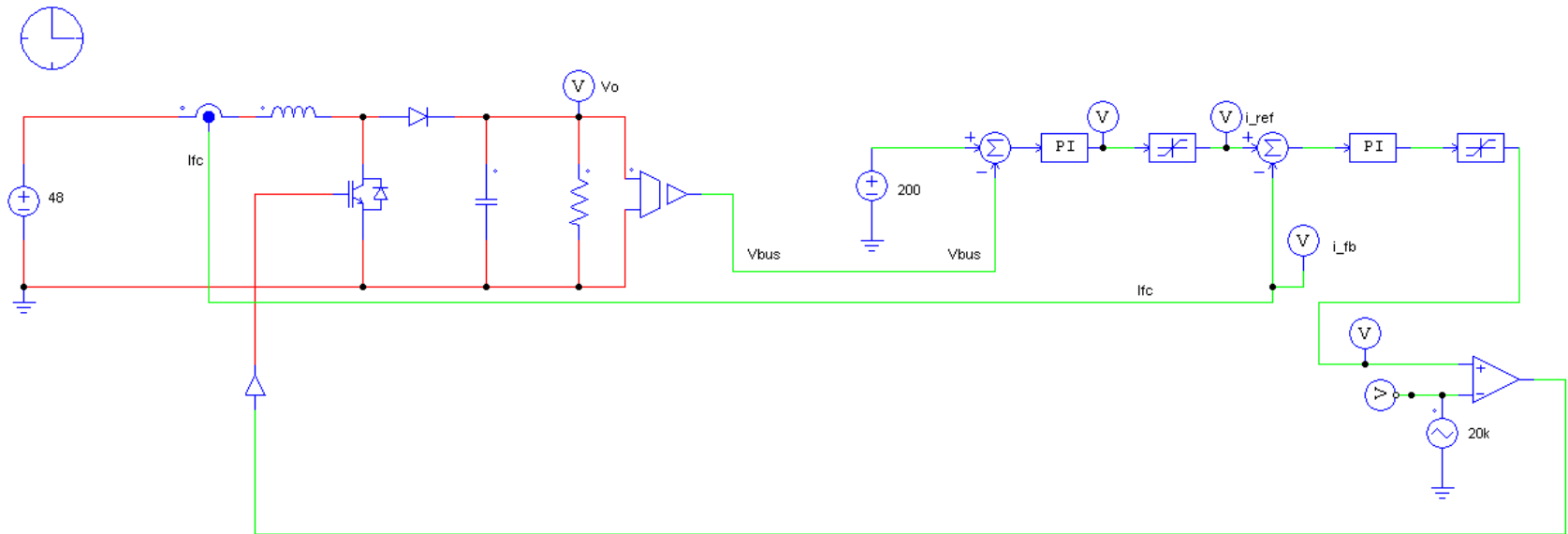


Boost Converter PI Control

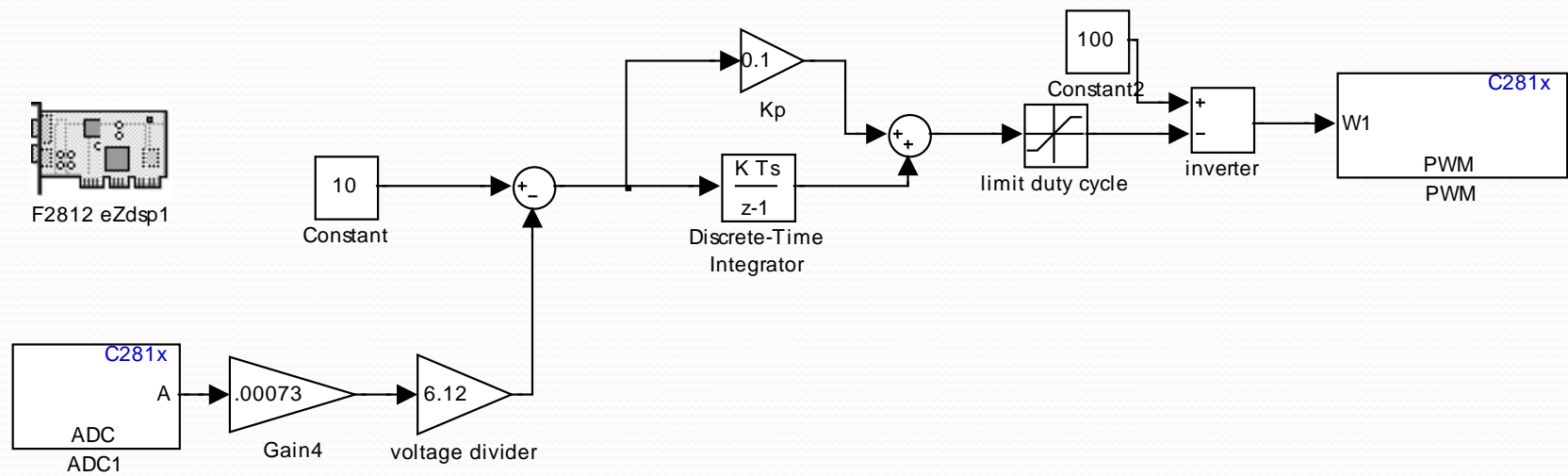


PI Control

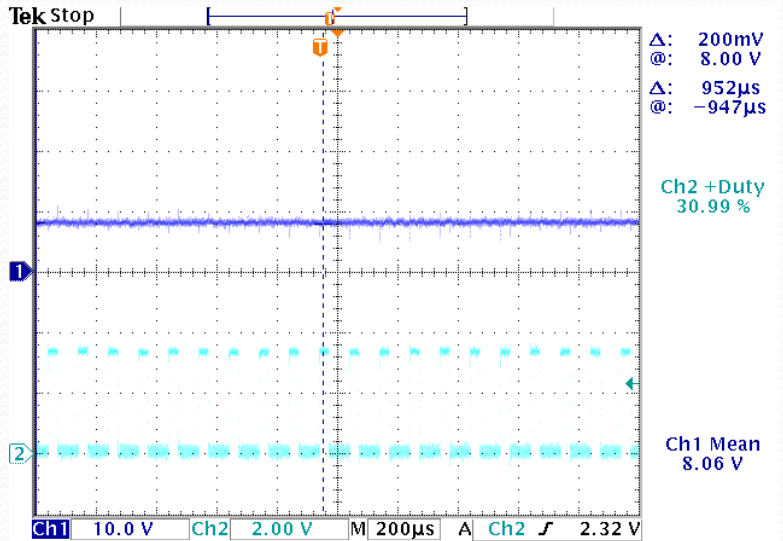


9 Feb 2012
10:54:39

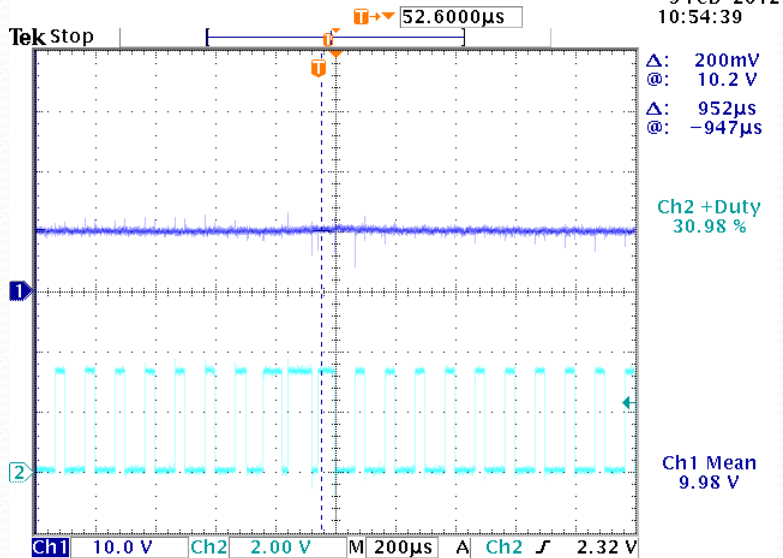

9 Feb 2012
10:55:13

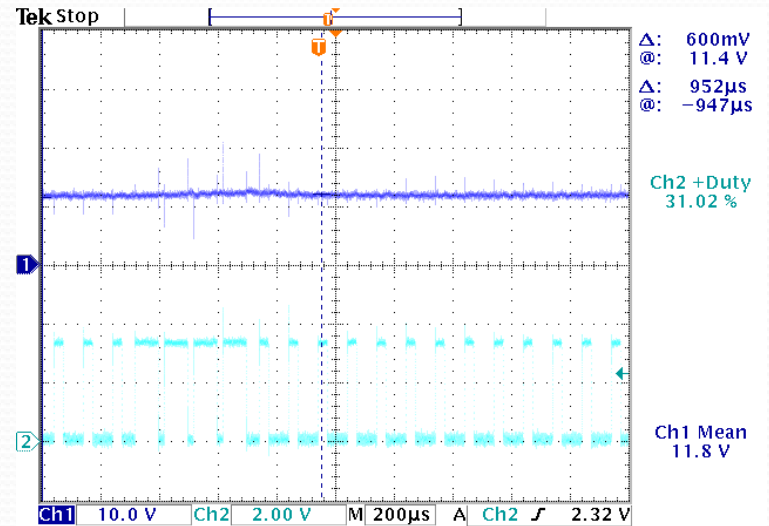


9 Feb 2012
10:56:17

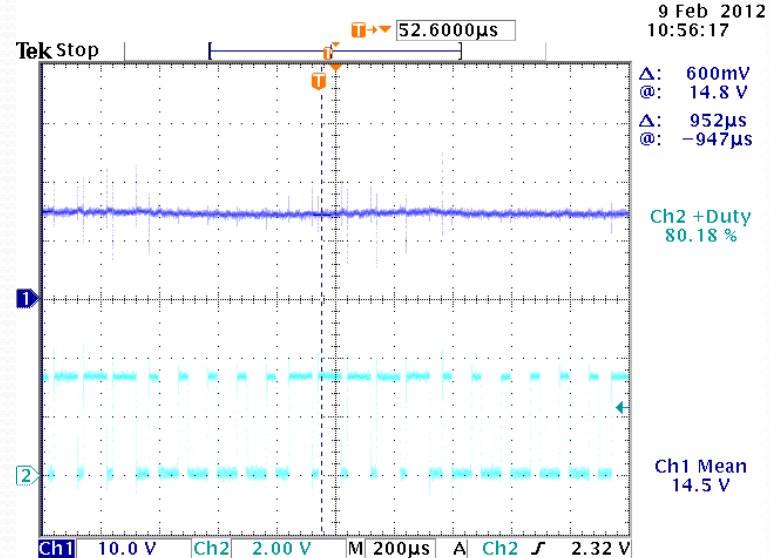


9 Feb 2012
10:56:46

Power Factor Correction

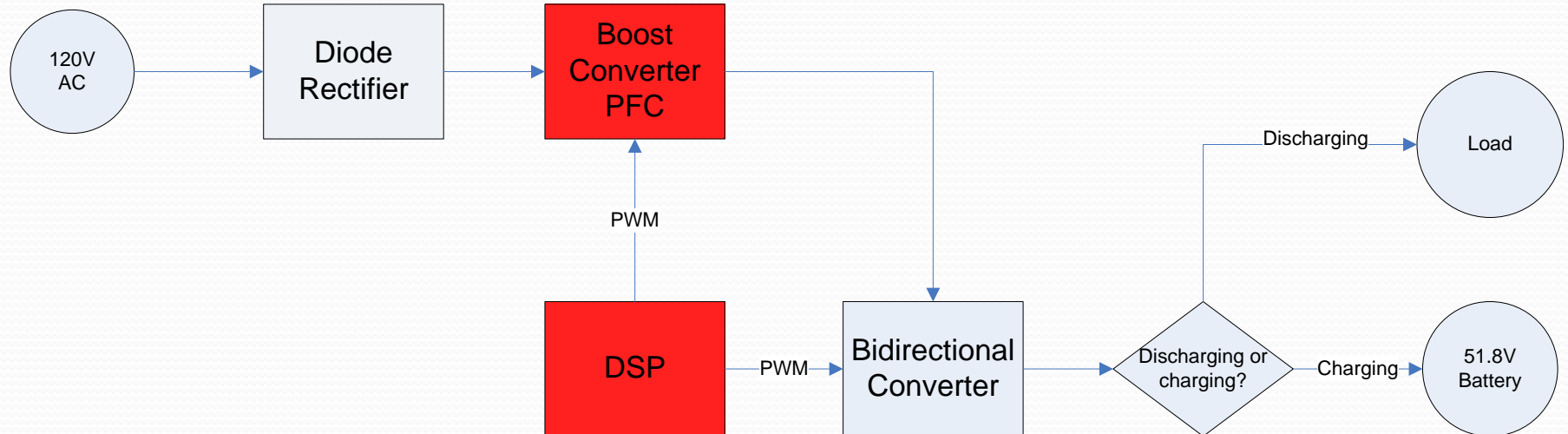

Power Factor Correction


- How it works:

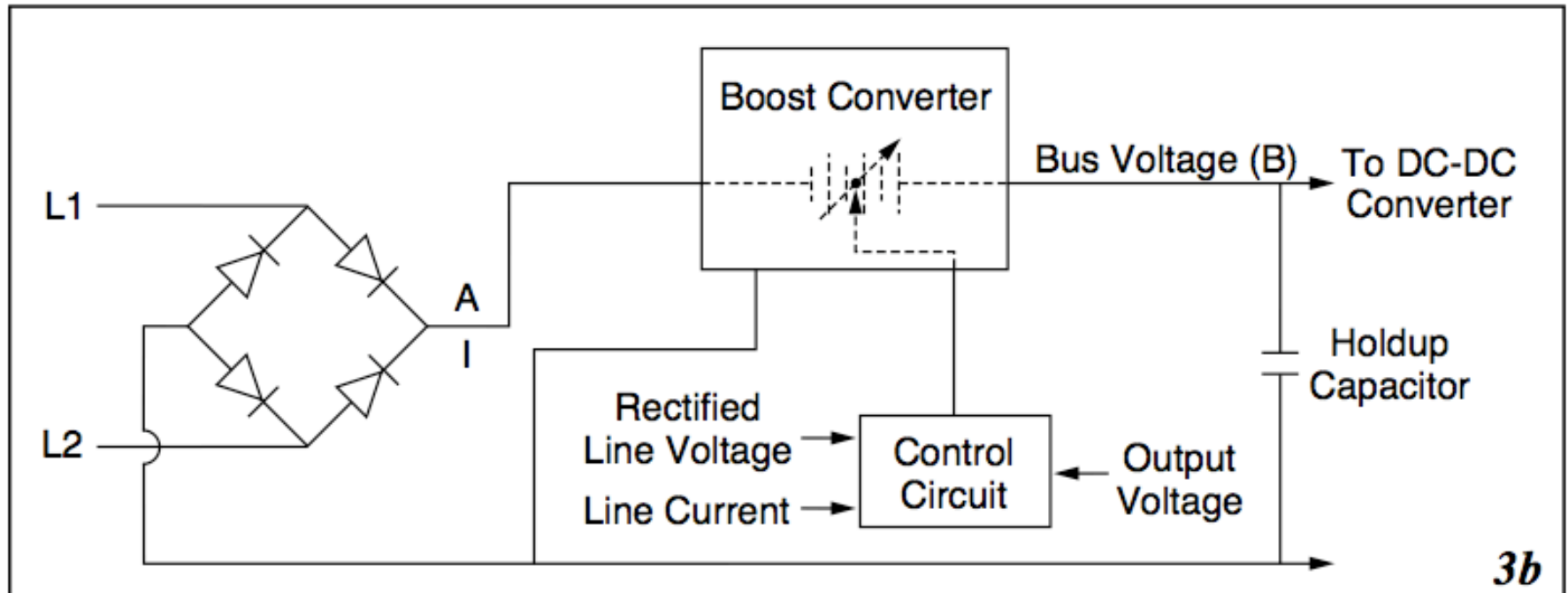


3b

Schematics

Power Factor Correction

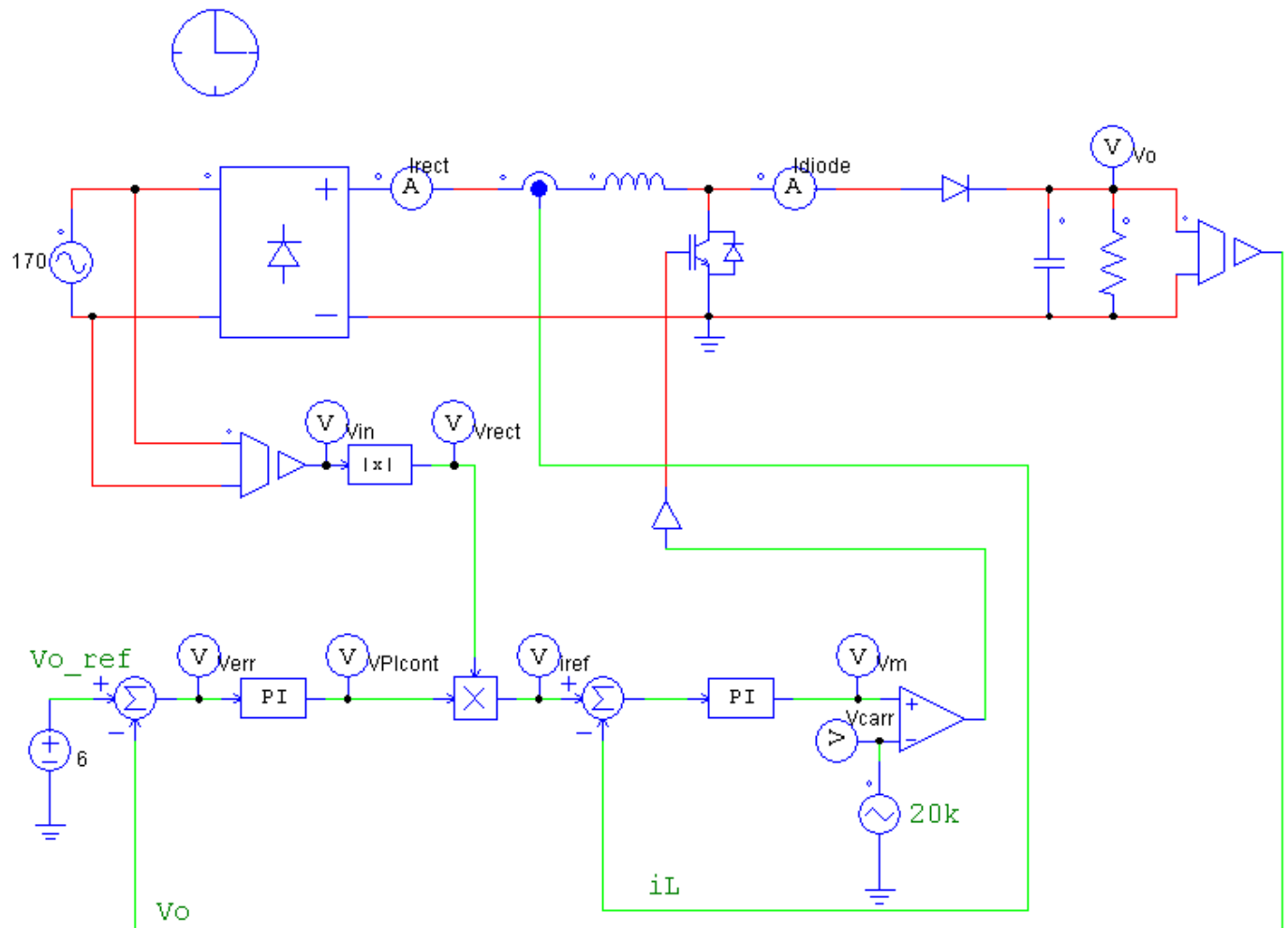


PFC Testing

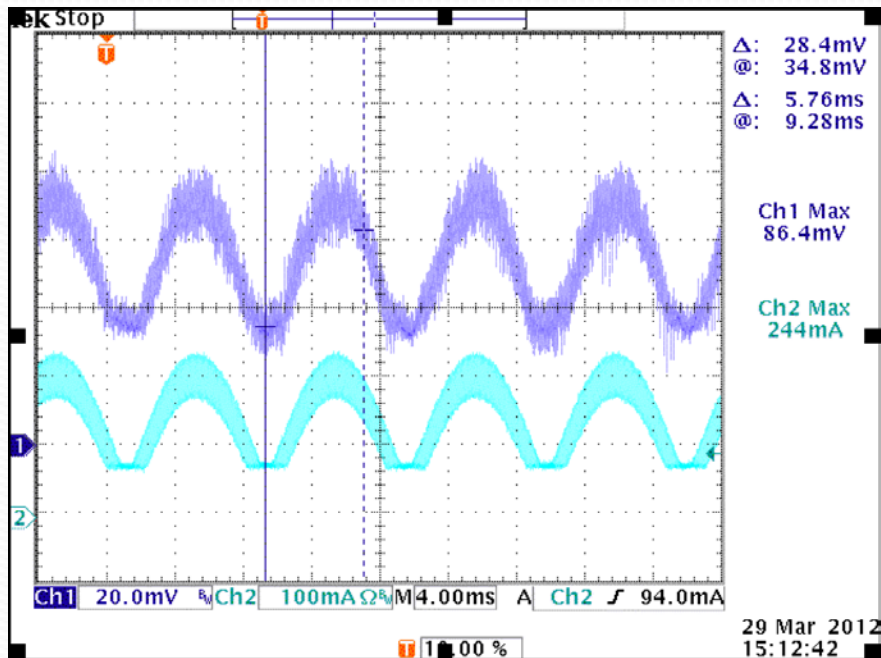

- Channel 1: output of current sensing circuitry and op amp input to the dsp
- Channel 2: output of current probe



- Open loop control, 50% duty cycle
- 80mV out of the op amp can be converted by multiplying by the 1.25 voltage divider, then multiply by 50/4 for the current sensor, and divide by 5 to factor in the 5 loops around the current sensor gives you 250mV which the current probe is showing.

PFC Testing

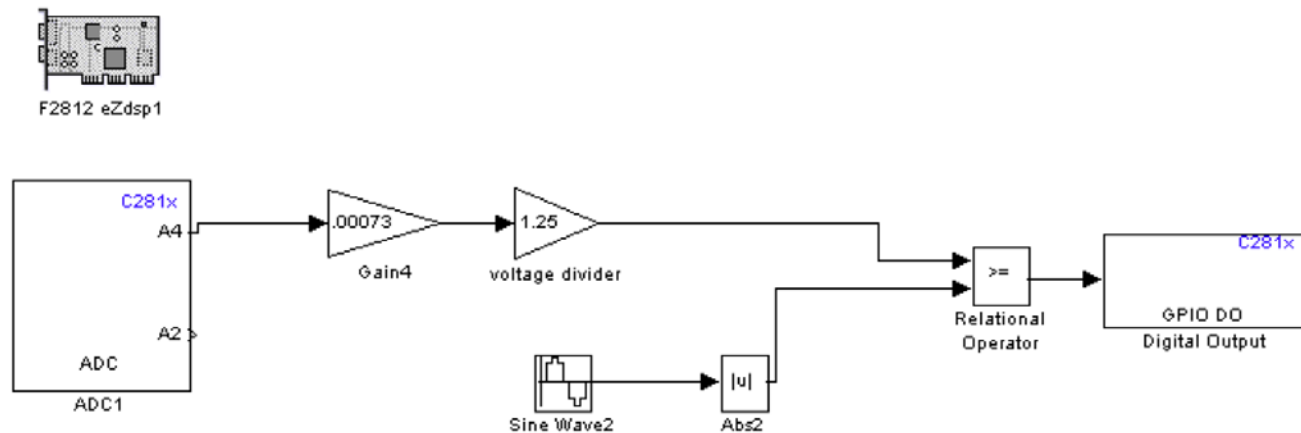

- Because the current being measured by the DSP is a rectified sign wave with an amplitude of approximately 80mV, I simulated this in Simulink as the reference current to match.

PFC Testing

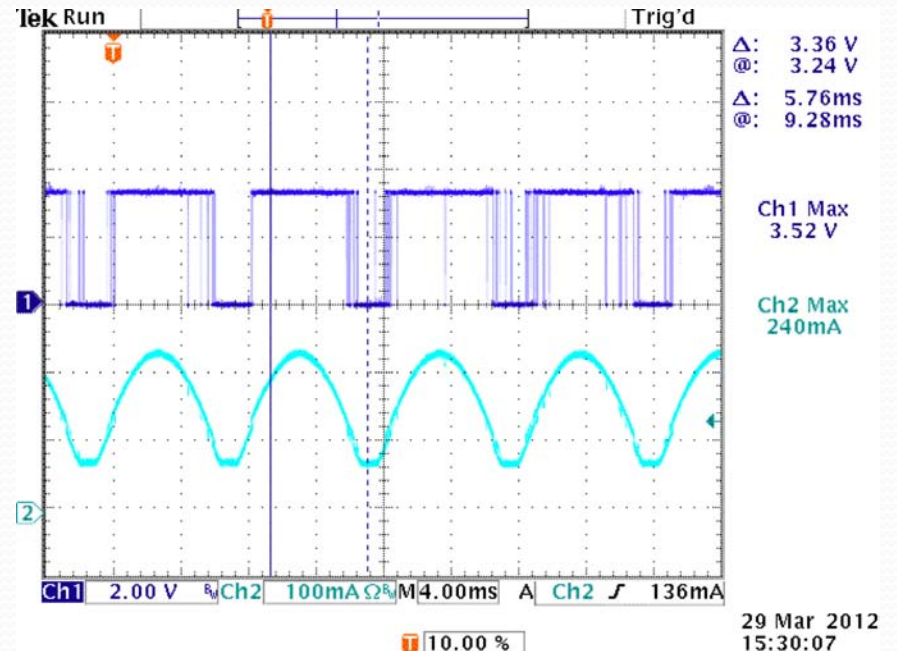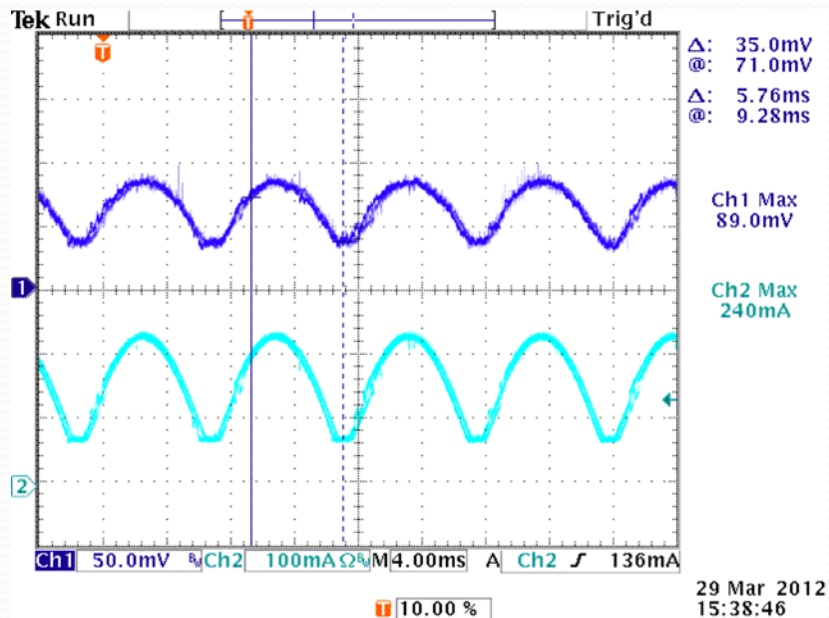


- 1: output of current sensing circuit opamp into DSP
- 2: current probe measuring current through inductor

- 1: constantly adjusting pwm

PFC PI Control




F2812 eZdsp1

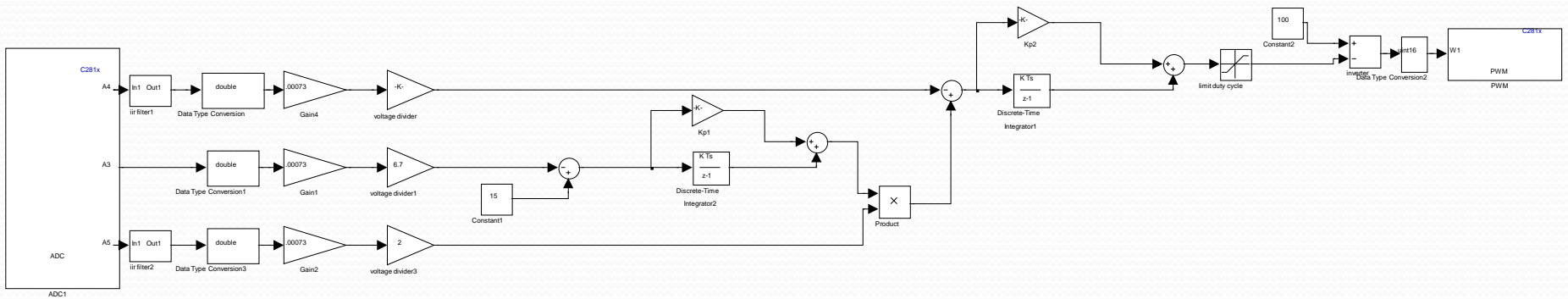


PFC PI Control


- Circuit in discontinuous mode

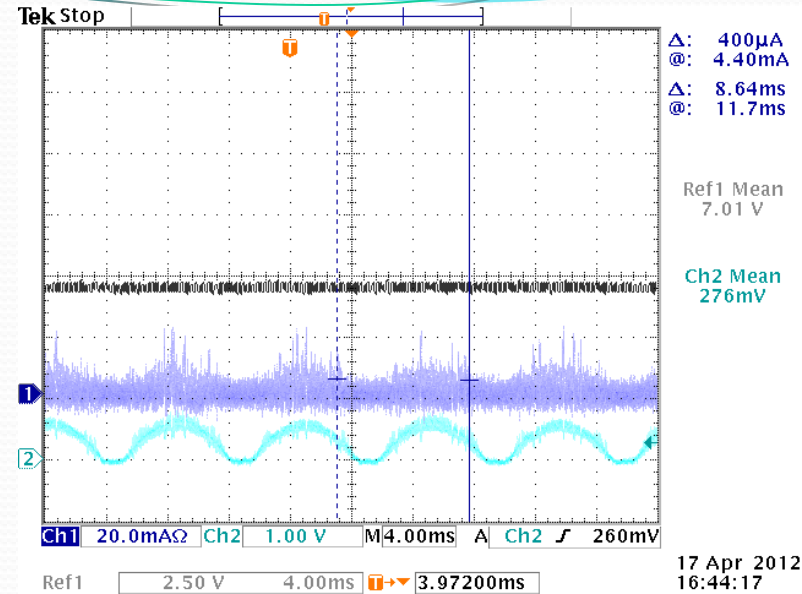

17 Apr 2012
16:44:17

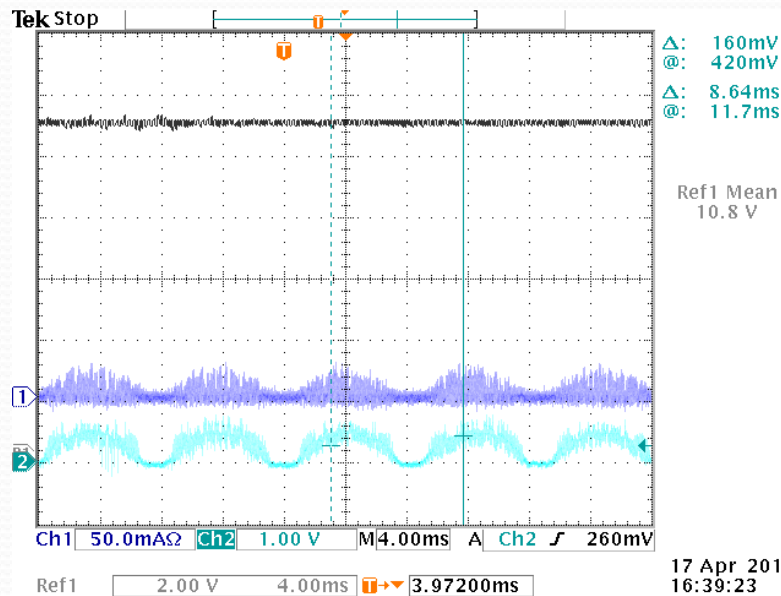

17 Apr 2012
16:39:23

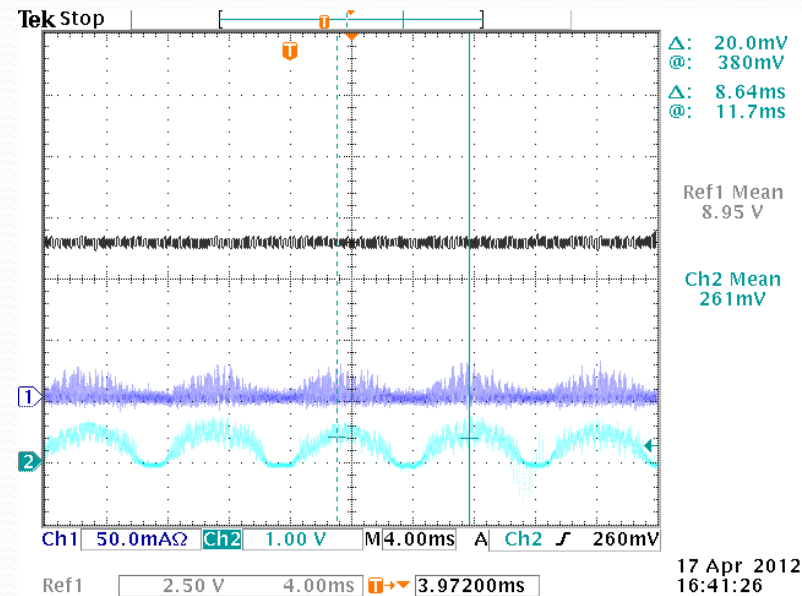

17 Apr 2012
16:41:26

Completed Work

- Designed full scale system
- Controls functioning
 - Full scale boost converter
 - Full scale buck converter
 - Small scale PFC

Future

- Use system to charge battery
- Acquire detailed parameters for battery
- Discharge battery through inverter to run a variable load
- Implement regenerative braking
- Utilize ultra-capacitors for regenerative braking energy storage



Questions?

Converter Equations

Capacitor and Inductor
Calculation Equations for
PFC and Bi-Directional
Converter

$$L = \frac{V_{out}}{4 f_{swi} \max \Delta I}$$

$$C = \frac{V_M I_M}{2 \Delta V_{out} \omega V_{out}}$$

Boost Converter

$$\frac{V_o}{V_i} = \frac{1}{1 - D}$$

Voltage Divider

$$V_{out} = \frac{R2}{R1 + R2} \cdot V_{in}$$

Buck Converter

$$\begin{aligned} (V_i - V_o)DT - V_o(1 - D)T &= 0 \\ \Rightarrow V_o - DV_i &= 0 \\ \Rightarrow D &= \frac{V_o}{V_i} \end{aligned}$$

Controller Equations

$$\frac{\tilde{v}_o}{\tilde{d}} = \frac{V_{in}}{LC} \frac{1 + srC}{s^2 + s\left(\frac{1}{RC} + \frac{r}{L}\right) + \frac{1}{LC}} \quad (\text{Buck})$$

$$\frac{\tilde{v}_o}{\tilde{d}} = \frac{V_{in}}{(1-D)^2} \left(1 - s\frac{L_e}{R}\right) \frac{1 + srC}{L_e C \left(s^2 + s\left(\frac{1}{RC} + \frac{r}{L_e}\right) + \frac{1}{L_e C}\right)} \quad (\text{Boost})$$

$$|G_L(s)|_{f_c} = |G_C(s)|_{f_c} \times |G_{PWM}(s)|_{f_c} \times |G_{PS}(s)|_{f_c} \times k_{FB} = 1$$

$$K_{boost} = \sqrt{\frac{\omega_p}{\omega_z}} \quad K_{boost} = \tan\left(45^\circ + \frac{\phi_{boost}}{4}\right)$$

$$f_z = \frac{f_c}{K_{boost}} \quad f_p = K_{boost} f_c$$

$$k_c = |G_C(s)|_{f_c} \frac{\omega_z}{K_{boost}}$$

$$\phi_{boost} = -90^\circ + \phi_{PM} - \angle G_{PS}(s)|_{f_c}$$

MOSFET vs. IGBT

