

Power Converters For An Electric Vehicle

Students


Jacob Anderson
Sam Emrie

Advisor

Dr. Woonki Na


Why the electric car?

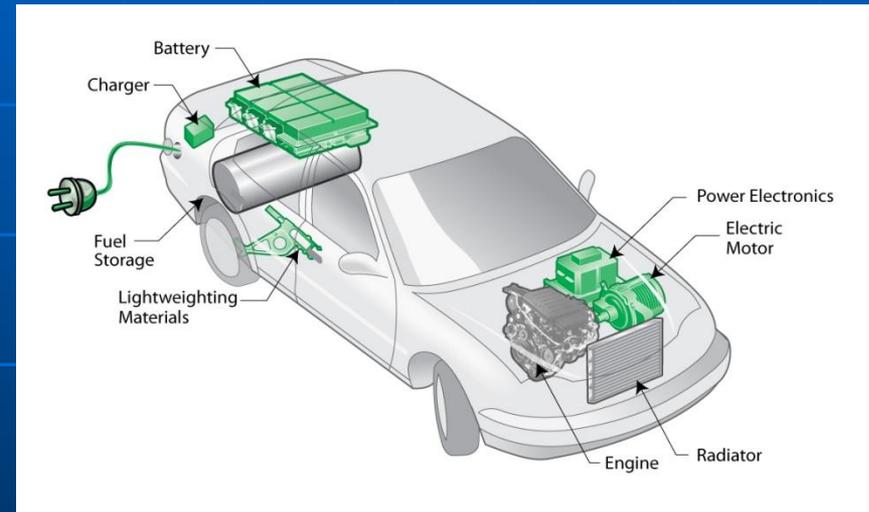- Improves fuel economy
- Reduces carbon emissions
- HEV vs PHEV



Electric Car Examples


Automotive Motor Drive Applications

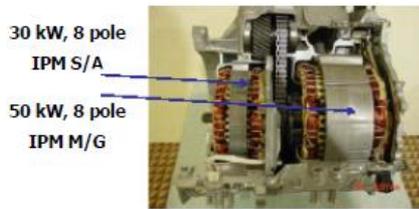

Toyota Prius Alternator and Traction Motor



Toyota Prius Power Conversion Box

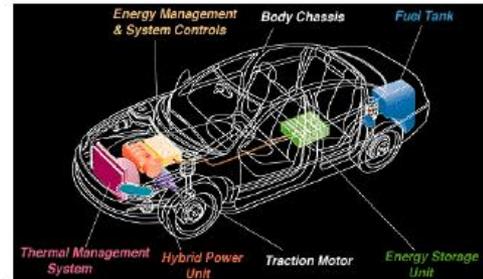

Ford Escape Hybrid



MSRP Range: \$26,780 - \$28,405

2.3 L, DOHC Engine
33 mpg (City)

Honda Civic



MSRP Range: \$19,650 - \$20,950

1.3 L, VTEC Engine
47 mpg (City)

Honda Insight



MSRP Range: \$19,180 - \$21,380

1.0 L, SOHC Engine
57 mpg (City)

Toyota Prius



MSRP: \$20,295

1.5 L, DOHC Engine
60 mpg (City)


Outline

- Brief Summary of Project
- Functional Description
 - System Block Diagram
 - Performances Specifications
- Battery Testing and DSP
- Results

Project Summary

- PFC Circuit (Power Factor Correction)
- Bidirectional Converter
- Battery Testing Circuit
- DSP Programming


System Block Diagram

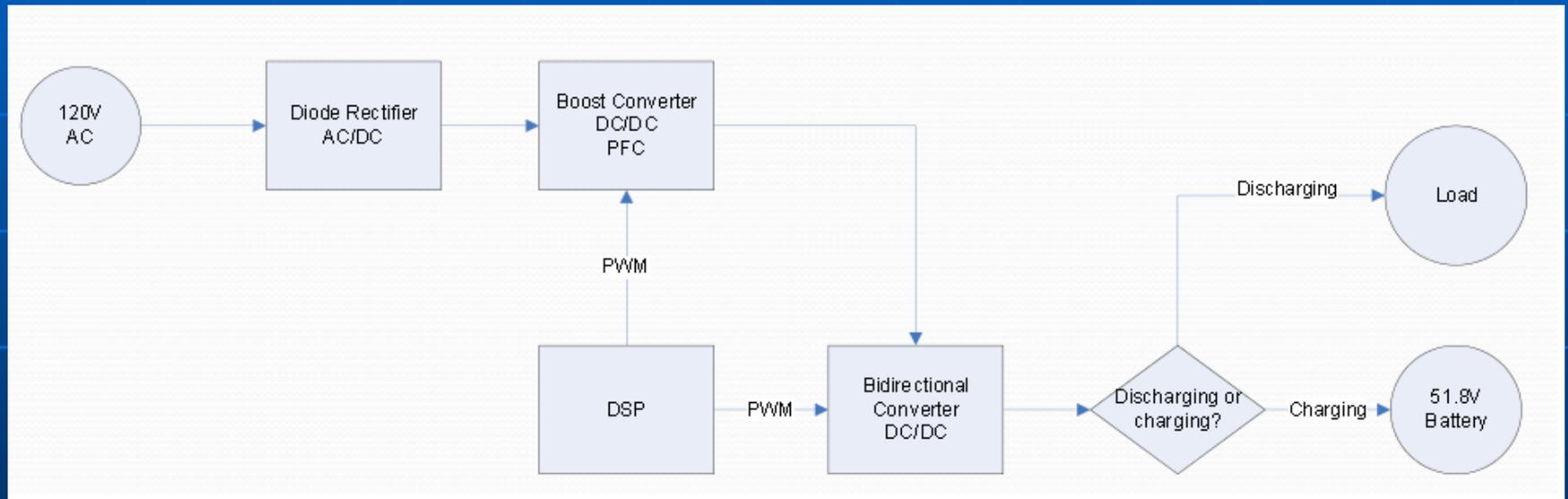

Why do we need PFC?


- Improves the efficiency of the system
- PHEV should control PFC
- Increase the amount of real power and reduce reactive power
- Use switch-mode boost converter

Power Factor Waveforms

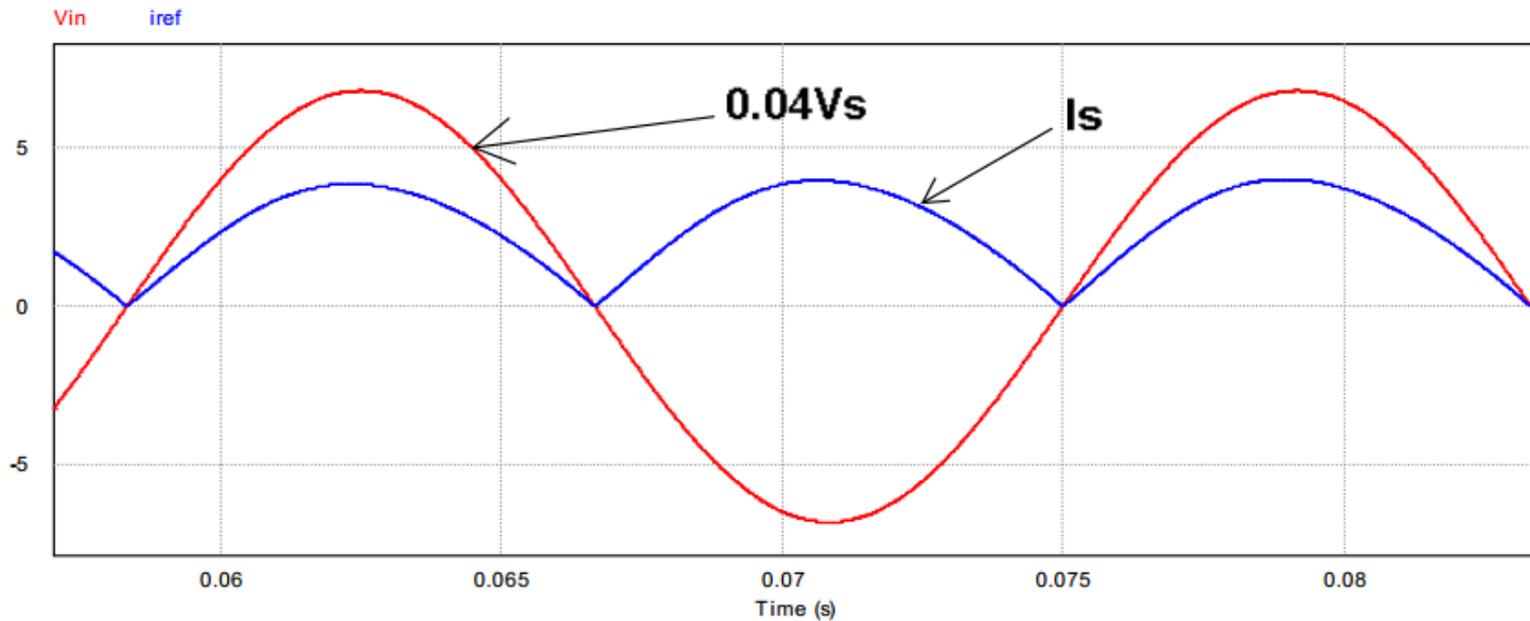


Designing The PFC Circuit

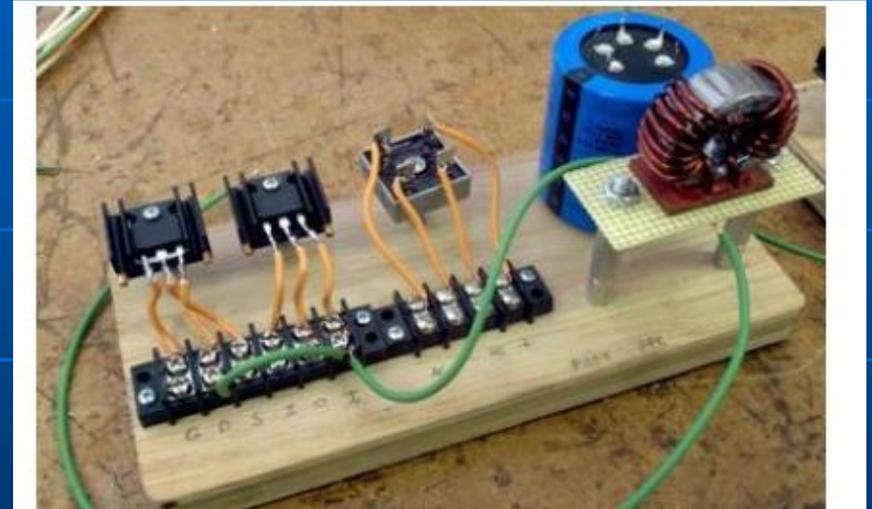- Re-made PFC Circuit
- Modified power diode to MOSFET
- Replaced Bridge Rectifier
- Circuit was tested using a IR2110



Control PFC Circuit

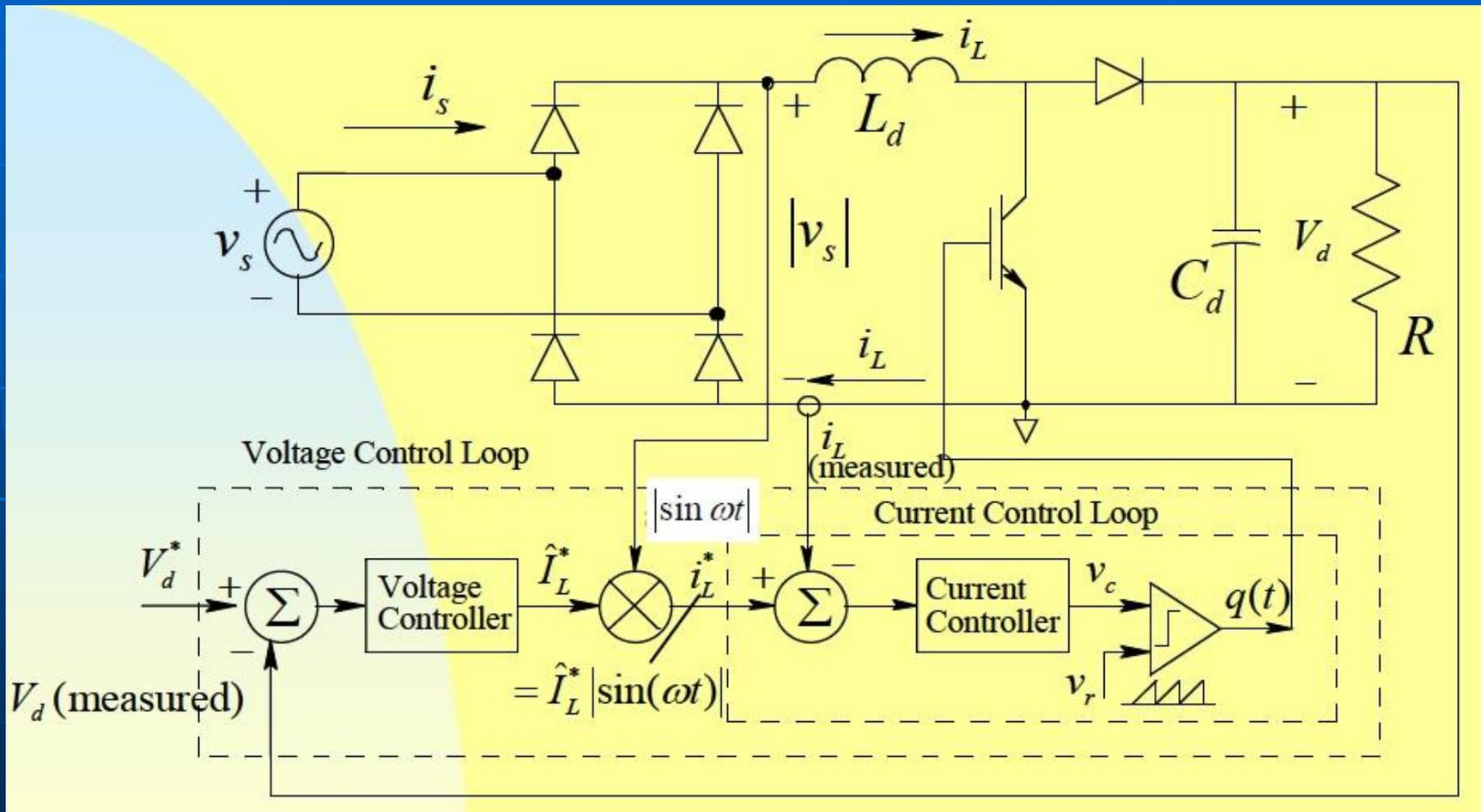


Transfer Function (PFC)


$$G_{ps_{pfc}} = \frac{\tilde{t}_L(s)}{\tilde{d}(s)} \cong \frac{V_o}{sL_d}$$

$$\frac{\tilde{V}_d}{\tilde{t}_L}(s) = \frac{1}{2} \frac{\hat{V}_s}{V_d} \frac{\frac{R}{2}}{1 + s \left(\frac{R}{2}\right) C}$$


Power Factor Correction

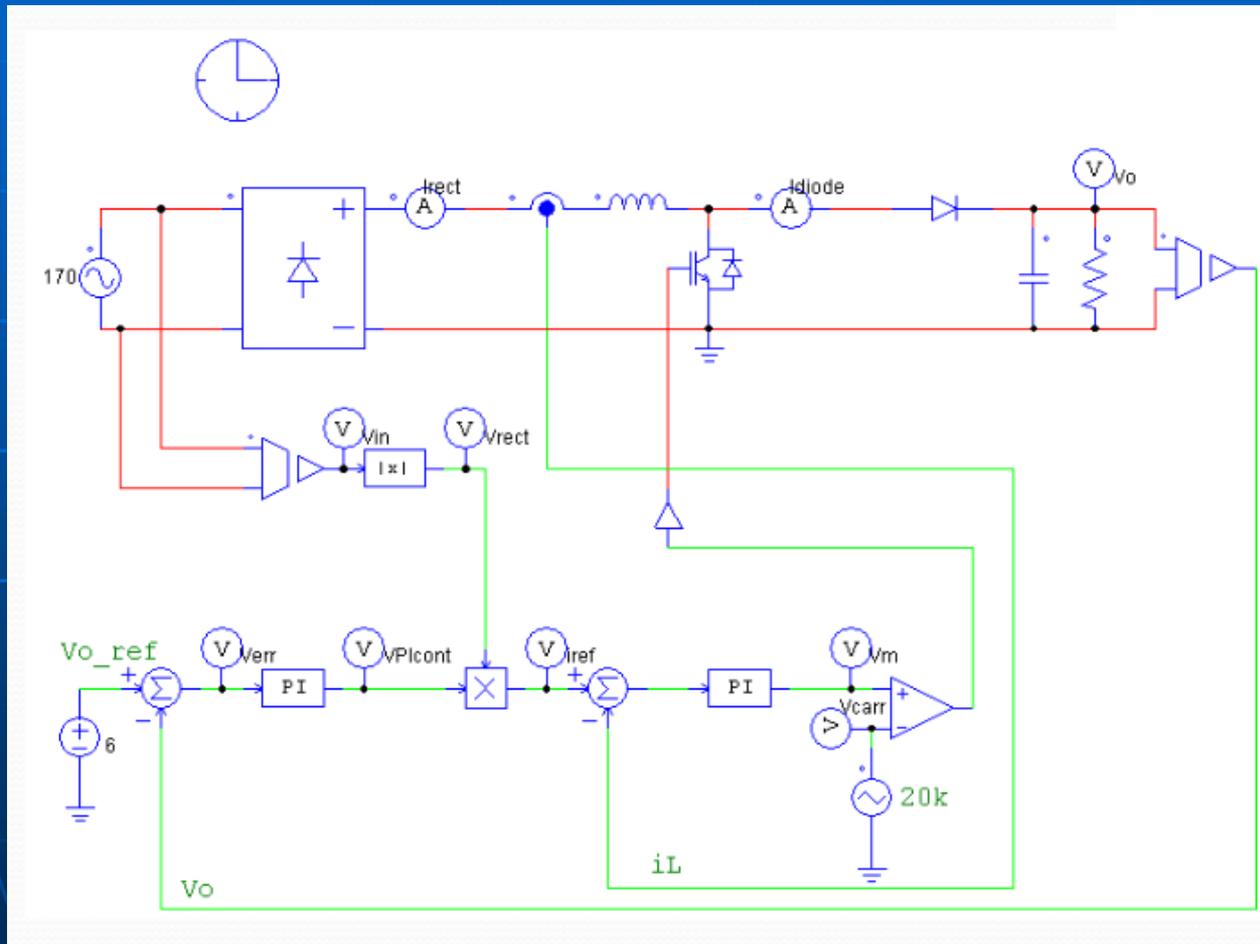



PFC PSIM Results

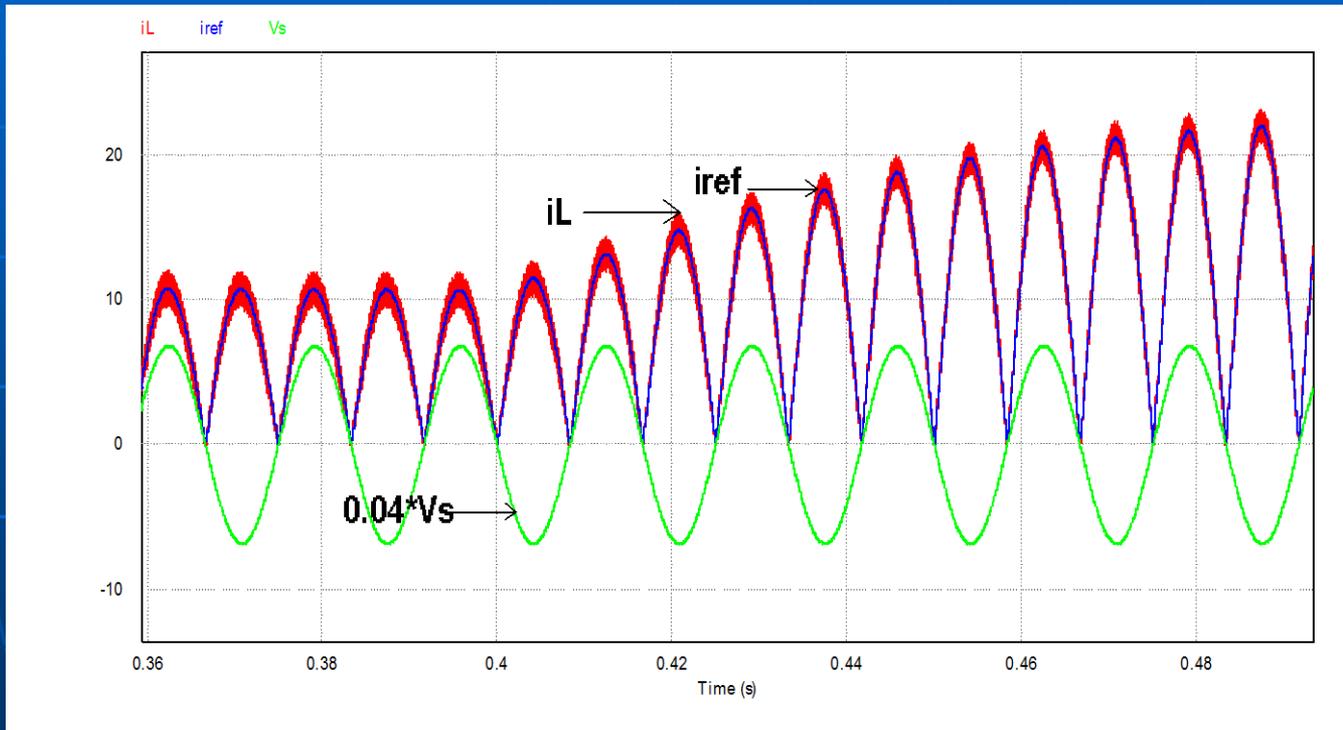

PFC Simulink Model

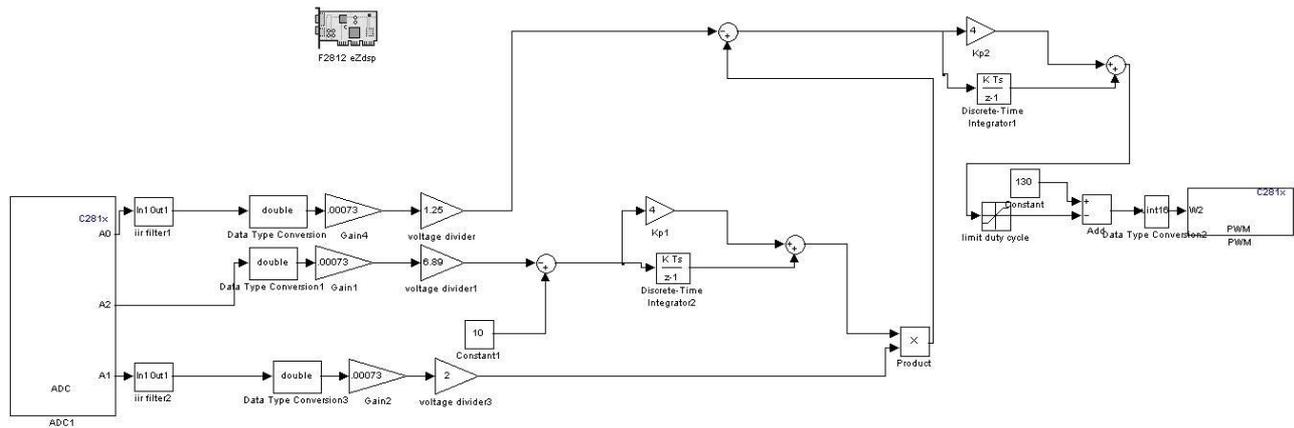


PFC Results

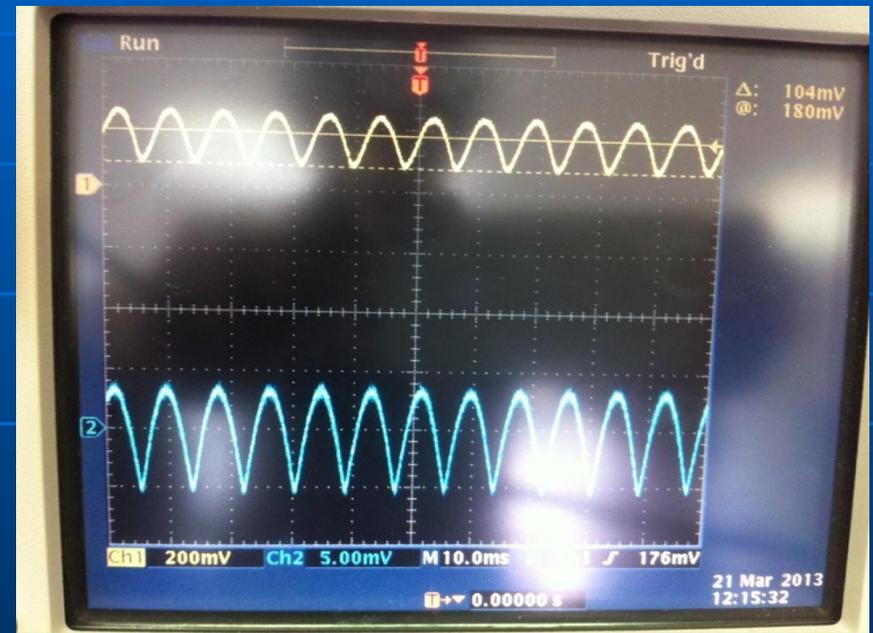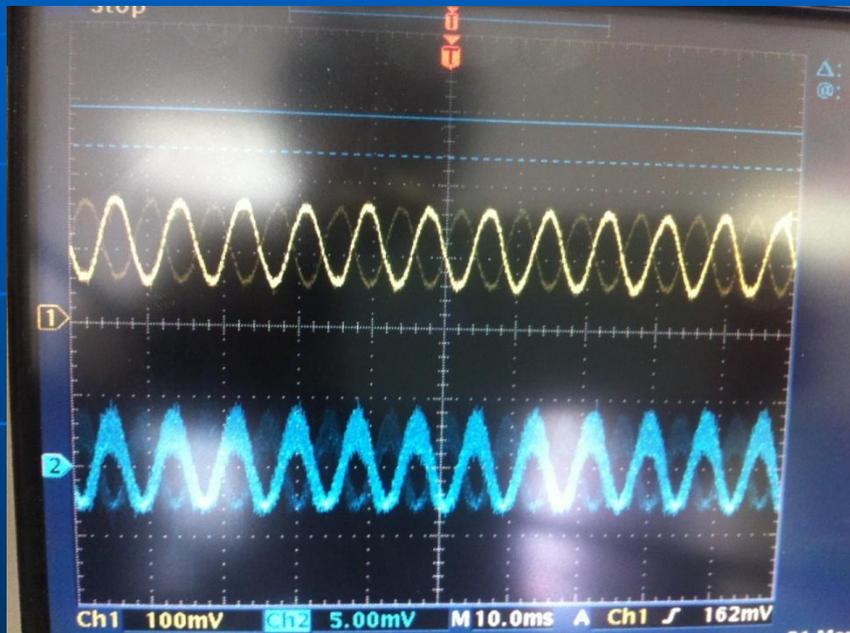

Why use a gate driver?

- Used as a medium between PWM output from the DSP and input from the high power circuit
- DSP does not supply enough voltage
- Gate driver physically switches the transistor
- Has it's own power supply to effectively output at a higher voltage

IR2110 Gate Driver Layout

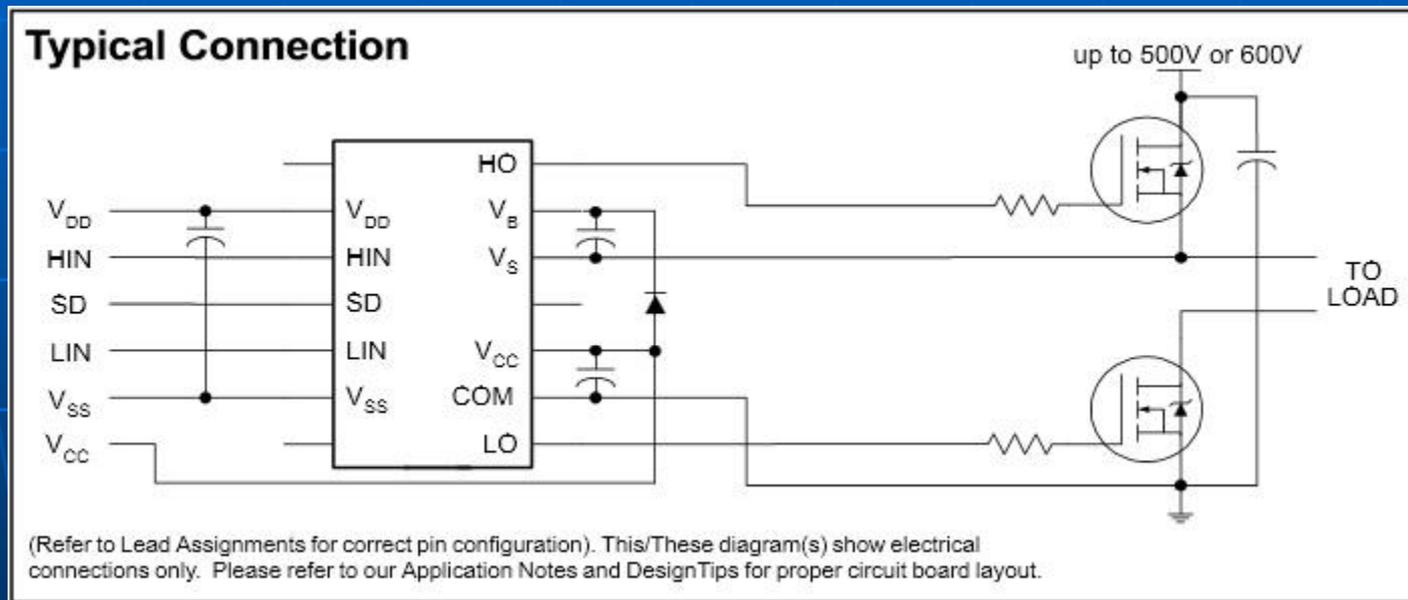

Testing With IR2110


- Previous group recommended IR2110
- Used to test battery, bi-directional, and PFC
- No Isolation

Testing With IR2181

- Similar problems to the IR2110
- The high side would not properly output
- Was hard to isolate circuit

HCPL-3180 Gate Driver

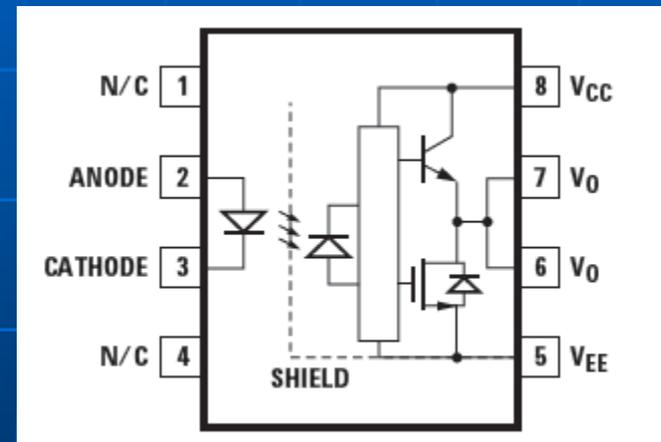- Easier to use due to being optically isolated
- Ideally suited for high frequency driving of power MOSFETS (2.5Amp)
- One gate driver is used per MOSFET




MOSFET

- IRFP460A N-Type
- $V_{DS} = 500V$
- $I_D = 20A$
- 55ns Rise Time
- High speed power switching




Bi-directional Converter

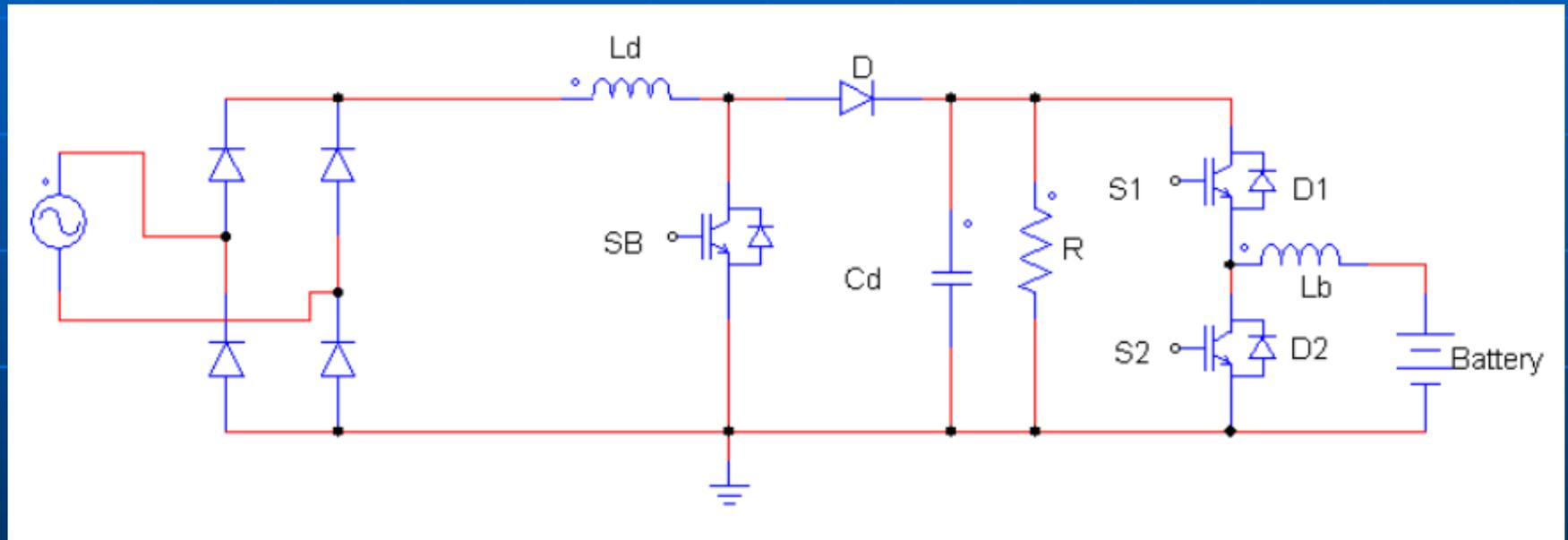

Designing The Bi-Directional Converter

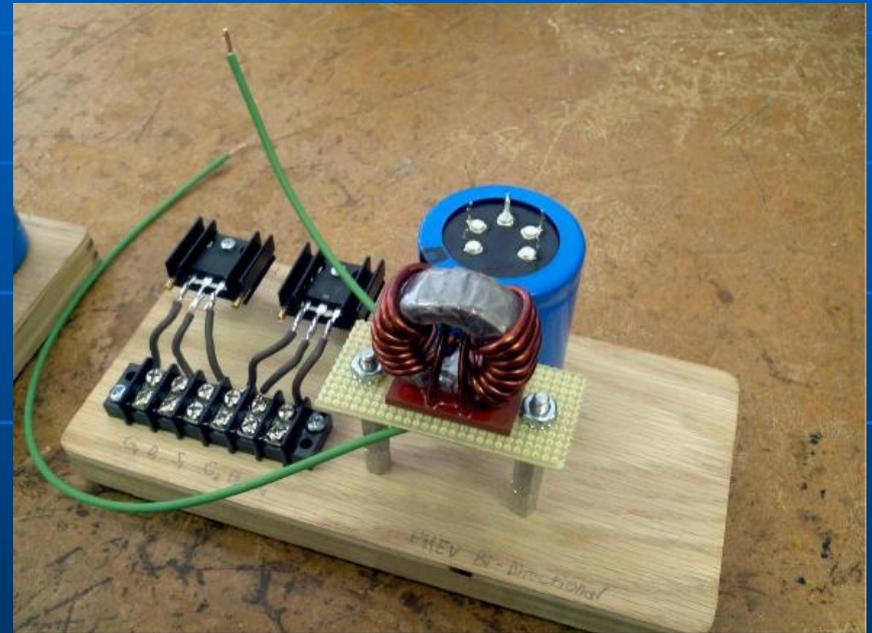- Redesigned from previous group's project
- Replaced the power diode with a MOSFET
- Circuit was tested using a HCPL-3180




L equations and C equations

$$\Delta V_o = (V_o(1 - D))/(8LCf^2)$$

$$\Delta i_L = V_o/L(1 - D)T_s$$


Buck Transfer Function

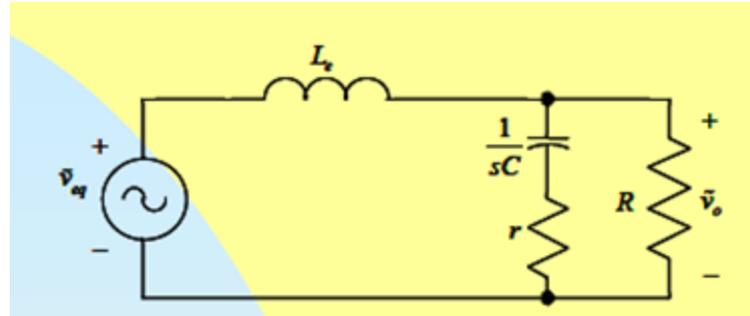

$$L_e = L \text{ (Buck)}$$

$$\frac{\tilde{v}_o}{\tilde{d}} = \frac{V_{in}}{LC} \frac{1 + srC}{s^2 + s \left(\frac{1}{RC} + \frac{r}{L} \right) + \frac{1}{LC}}$$

Buck Transfer Function Response

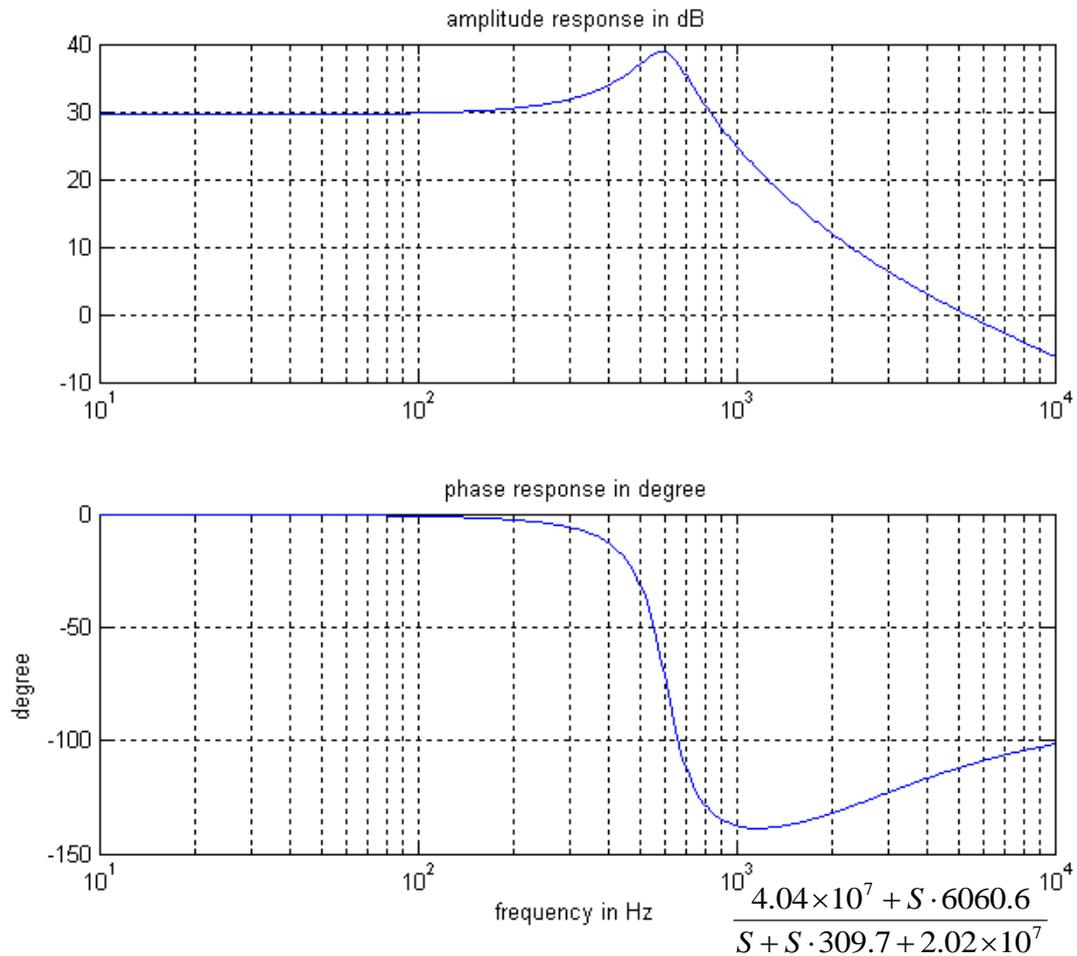

Buck Voltage Controller Equations

$$G_c(s) = \frac{sk_p + k_i}{s} \quad f_c > \frac{1}{2\pi\sqrt{LC}}$$

$$|G_c(s)|_{f_c} = \sqrt{k_p^2 + \left(\frac{k_i}{\omega}\right)^2}$$

$$\angle G_c(s)_{f_c} = \tan^{-1} \left(\frac{-\frac{k_i}{\omega}}{k_p} \right)$$

Buck Voltage Controller Equations

$$1 = |G_c(s)|_{f_c} \cdot |G_{pwm}(s)|_{f_c} \cdot |G_{ps}(s)|_{f_c} \cdot k_{fb}$$

$$1 = |G_c(s)|_{f_c} \cdot .263 \cdot 5.7 \cdot 1$$

$$\phi_{boost} = -90^\circ + \phi_{pm} - \angle G_{ps}(s)_{f_c}$$

$$k_p = .444 \quad k_i = 806.1$$

Buck Current Controller Equations

$$\phi_{boost} = -90^\circ + \phi_{pm} - \angle G_{ps}(s)_f$$


$$|G_c(s)| \times |G_{ps}(s)|_f = 1$$

$$\phi_{boost} + (-90^\circ) = \angle G_c$$

$$|G_c(s)|_f = \sqrt{k_p^2 + \left(\frac{k_i}{w}\right)^2}$$

$$\angle G_c(s)_f = \tan^{-1} \left(\frac{-\frac{k_i}{w}}{k_p} \right)$$

Buck Voltage Controller Equations

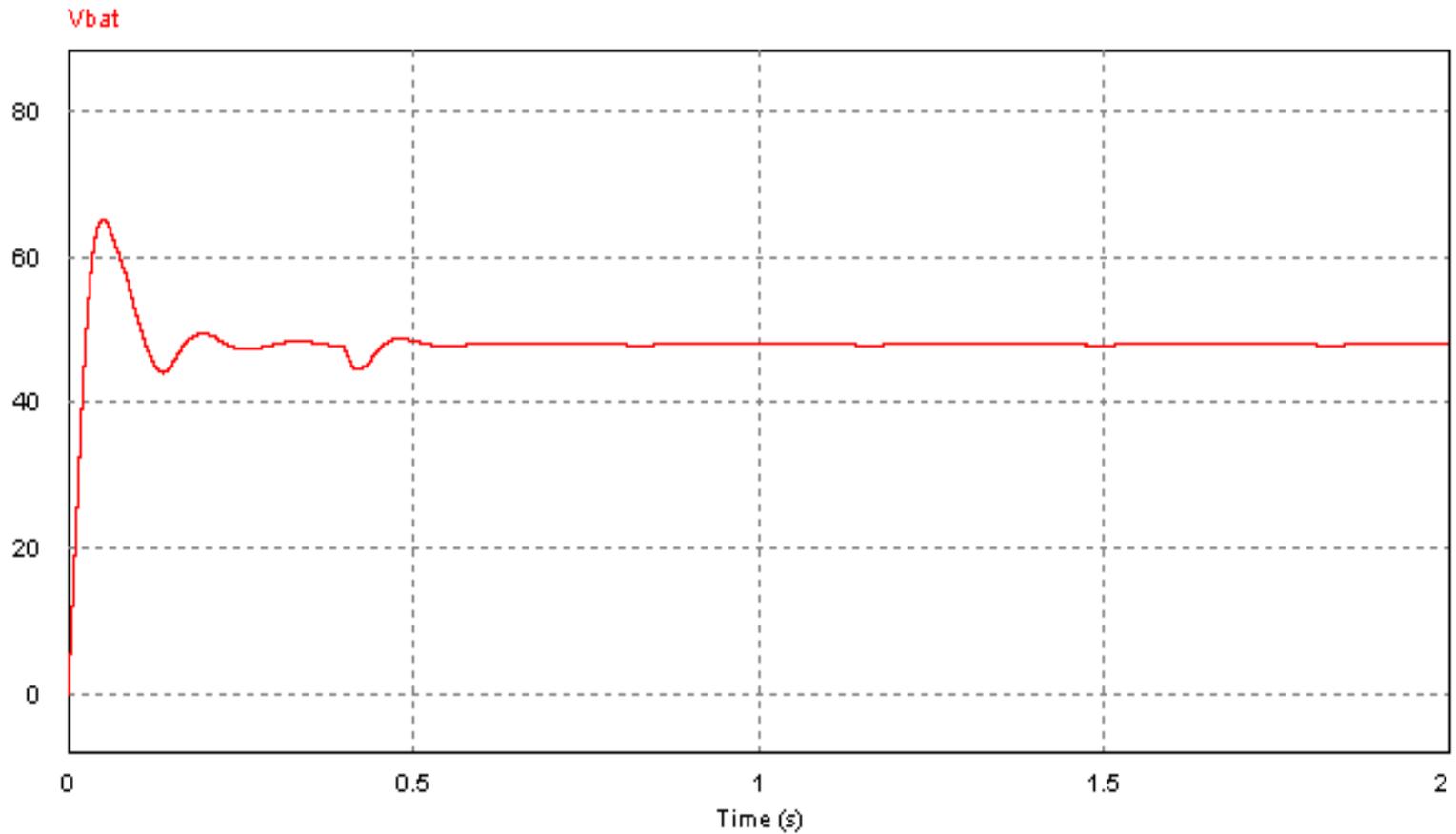

Battery Specs for Low and High Voltage


- 7.4V
- 3000 MilliWatt Hours




- 51.8V
- 10Amp-Hours
- Max Discharge Rate 40A




Battery Model

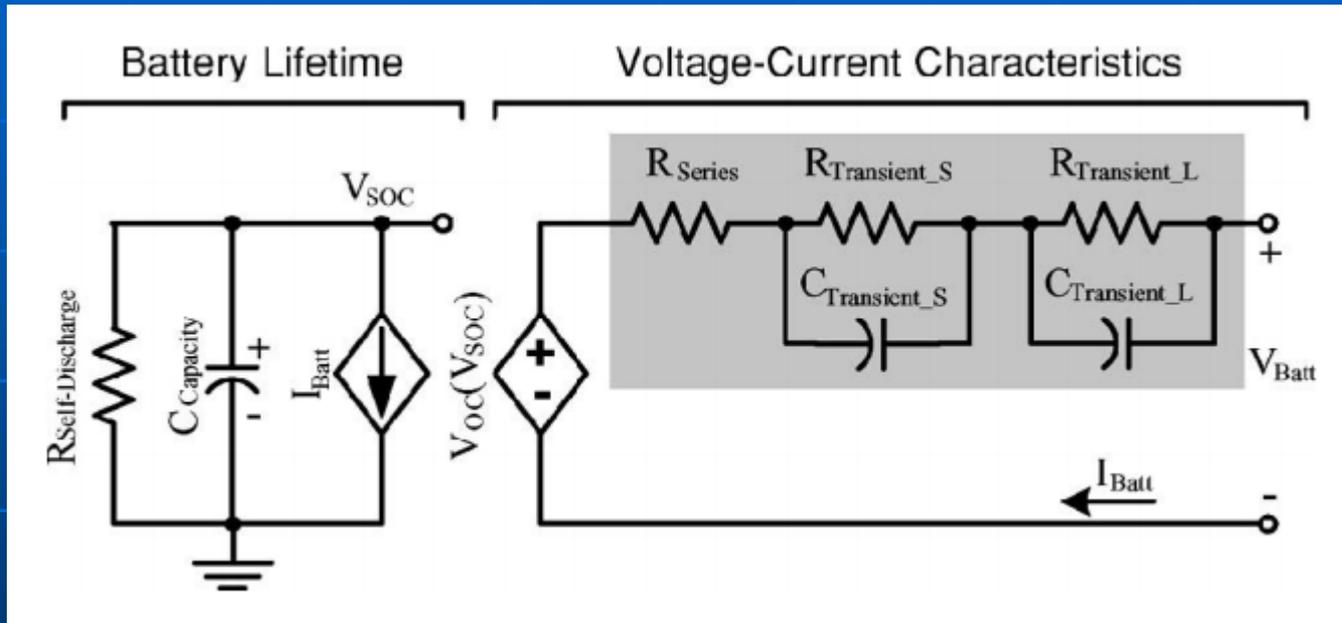

Battery Discharging Rate

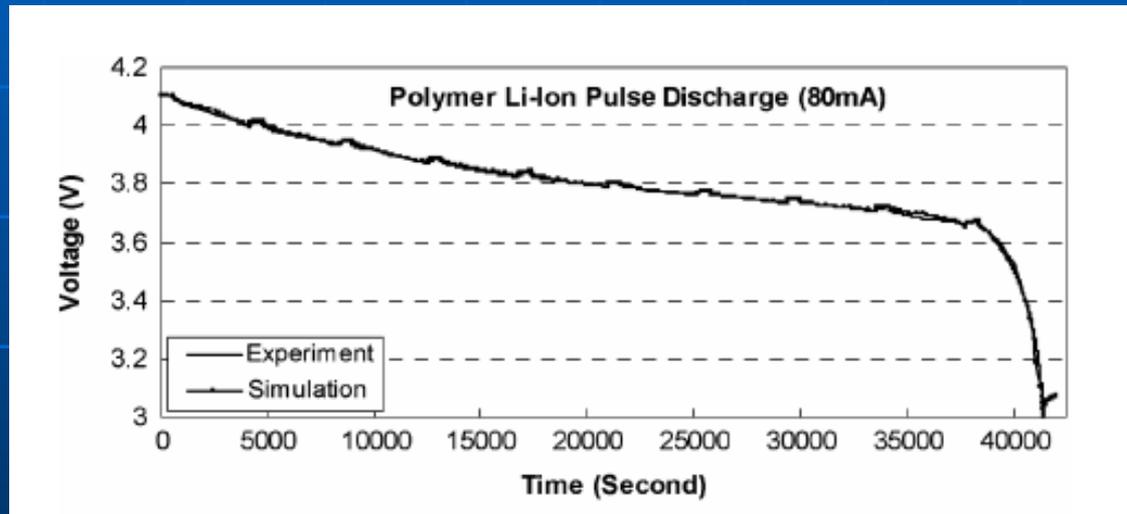

Battery Testing Circuit

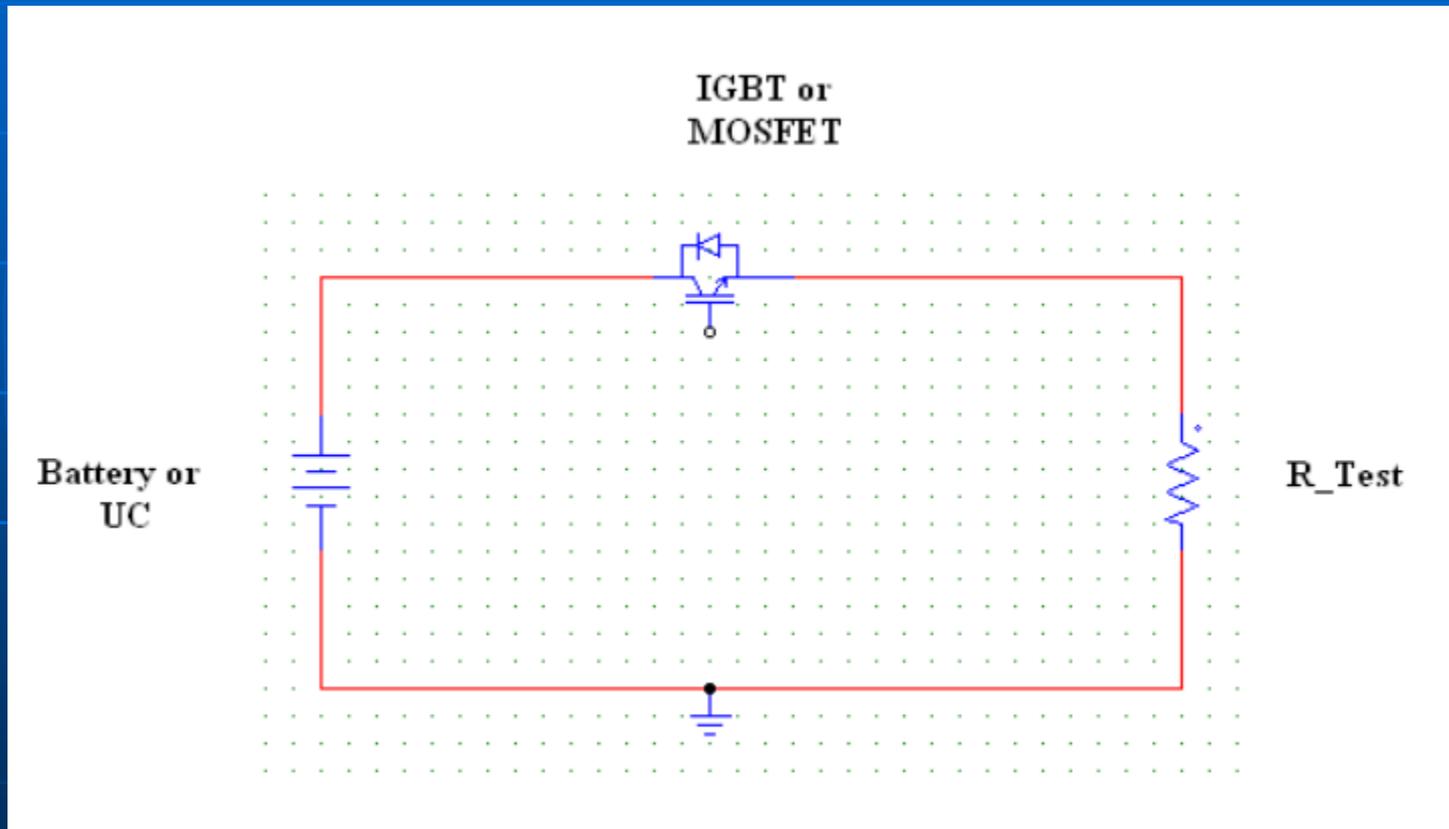


Battery Testing Circuit

- IR2110 used as gate driver
- G4PC30UD IGBT used
- 20ohm resistor used for small scale
- 100ohm resistor used for large scale


IGBT

- G4PC30UD IGBT used
- $V_{CES} = 600V$
- $V_{CE(on)} = 1.95V$
- @ $V_{ge} = 15V, I_c = 12A$
- Optimized for high operating frequencies



Battery Testing Small Scale

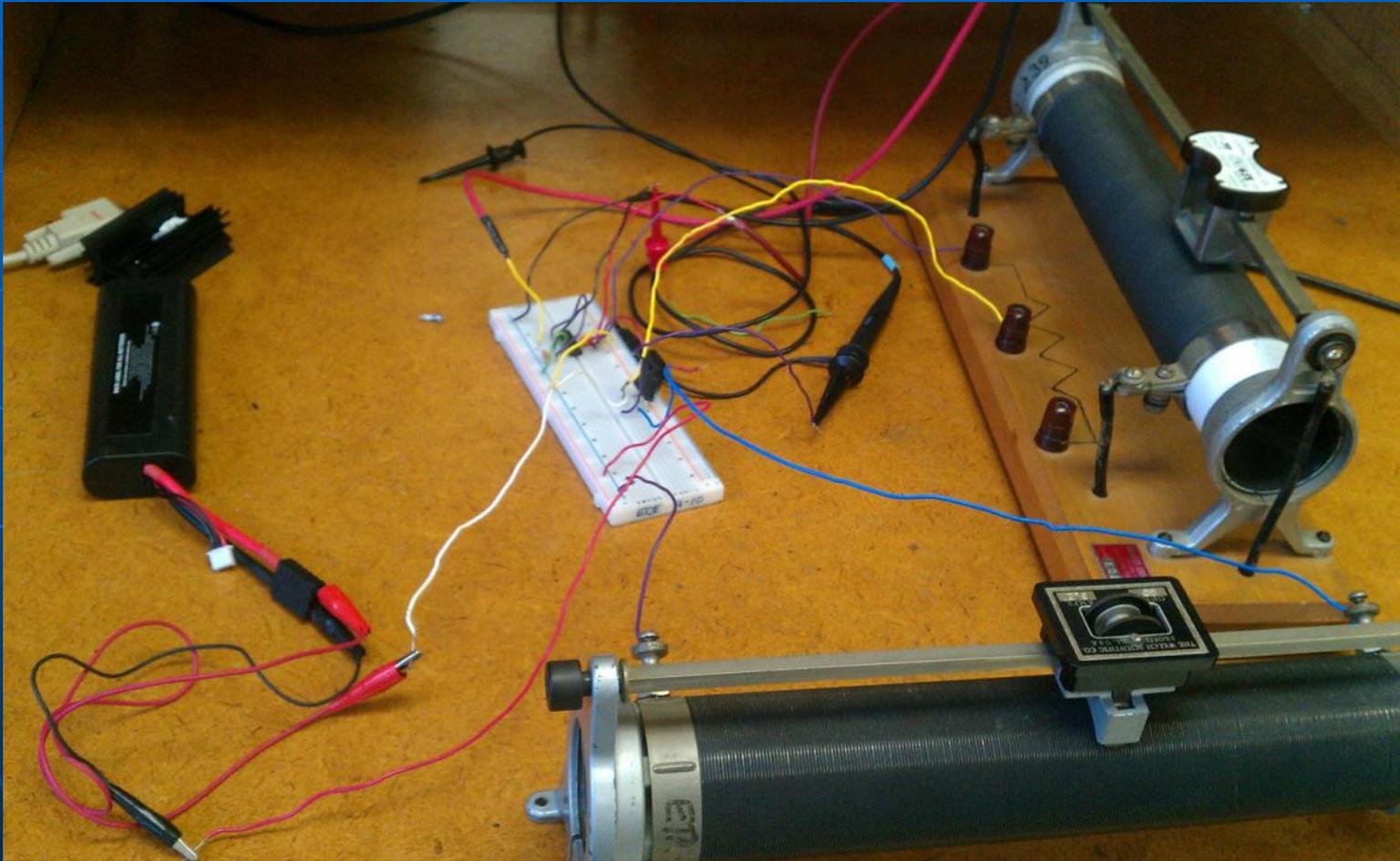


Small Scale Results

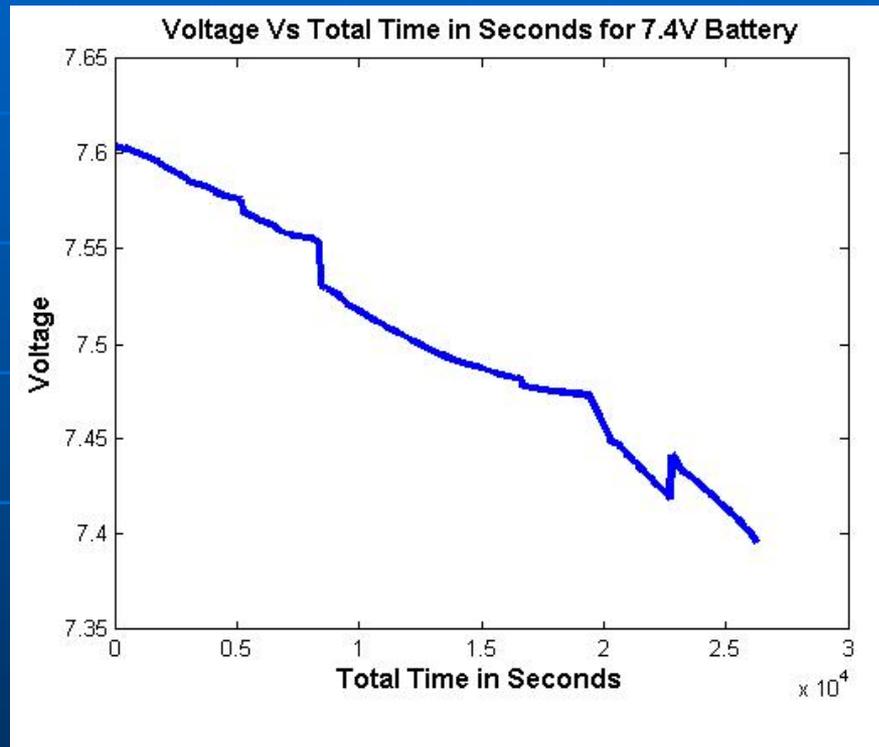

Comparison of Discharging Rate

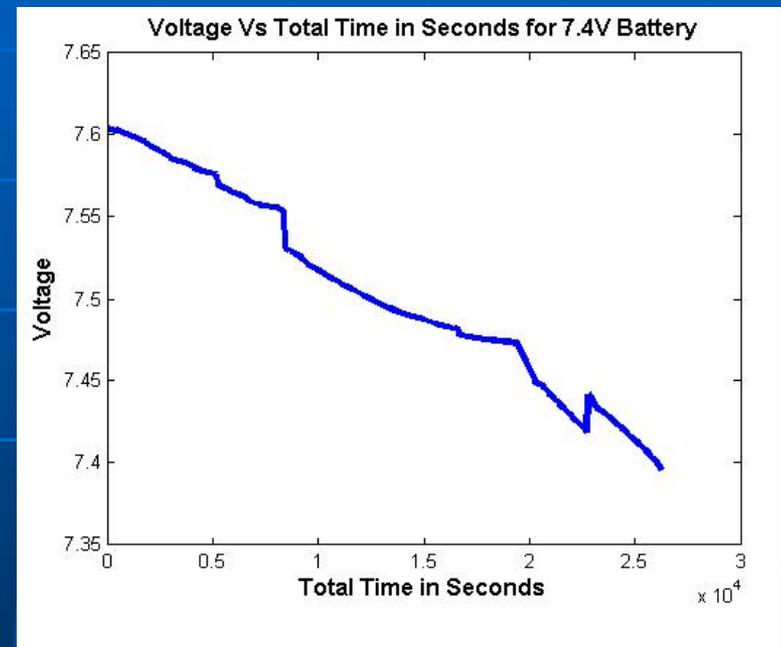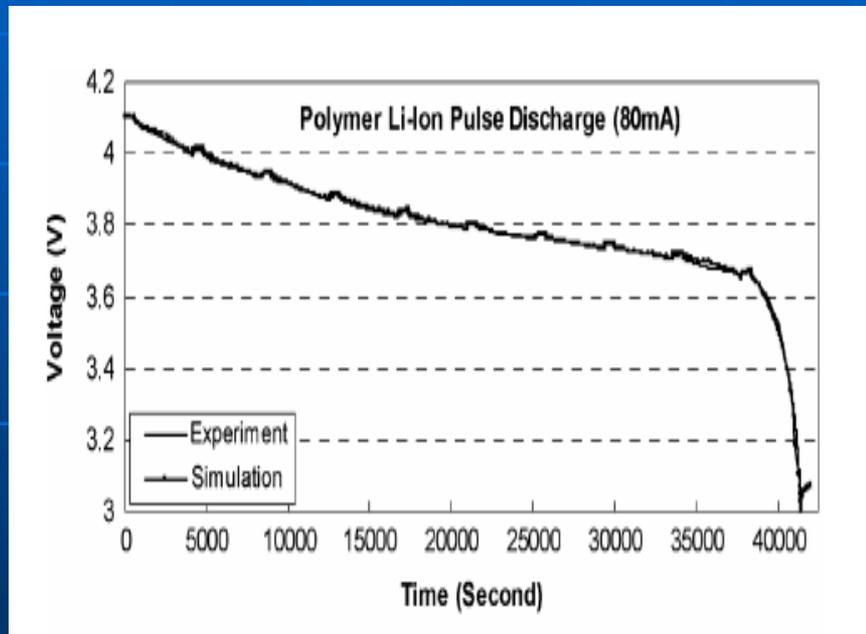

Discharging Rate of 51.8V Battery

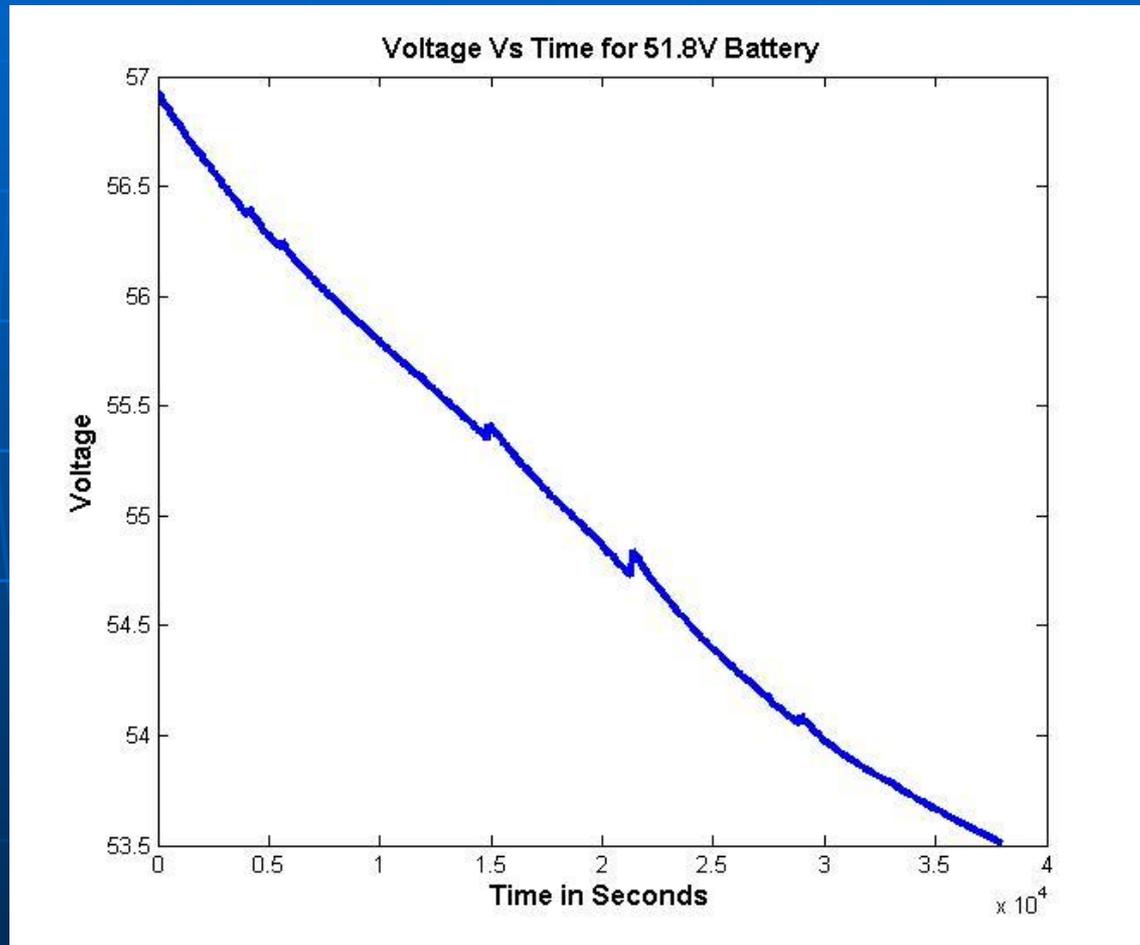

Equations

$$V_{oc}(SOC) = -1.031e^{-35 \cdot SOC} + 3.685 + 0.2156 \cdot SOC - 0.1178 \cdot SOC^2 + 0.3201 \cdot SOC^3$$

$$R_{Series}(SOC) = 0.1562 \cdot e^{-24.37 \cdot SOC} + 0.07446$$


$$R_{Transient_s}(SOC) = 0.3208 \cdot e^{-29.14 \cdot SOC} + 0.04669$$

$$C_{Transient_s}(SOC) = -752.9 \cdot e^{-13.51 \cdot SOC} + 703.6$$


$$R_{Transient_L}(SOC) = 6.603 \cdot e^{-155.2 \cdot SOC} + 0.04984$$

$$C_{Transient_L}(SOC) = -6056 \cdot e^{-27.12 \cdot SOC} + 4475$$


Soft Model

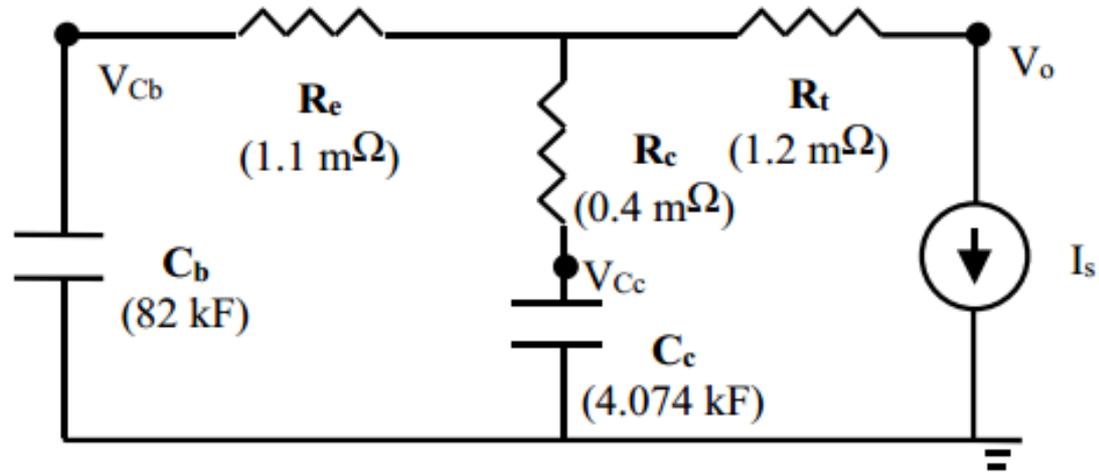


Soft Model

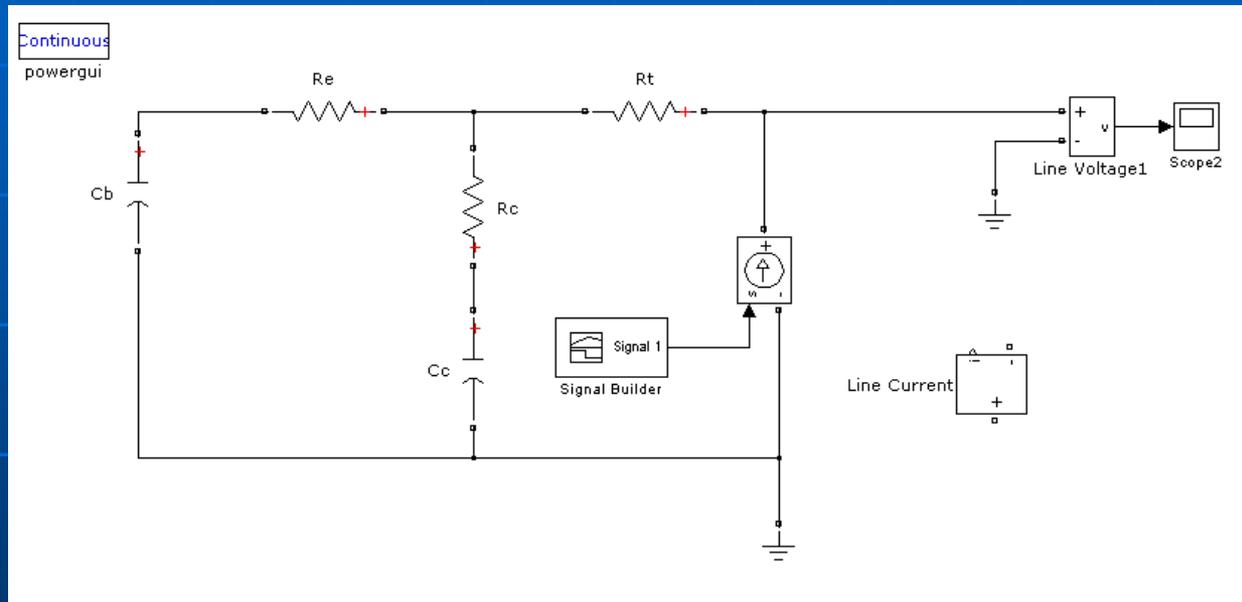


Charging

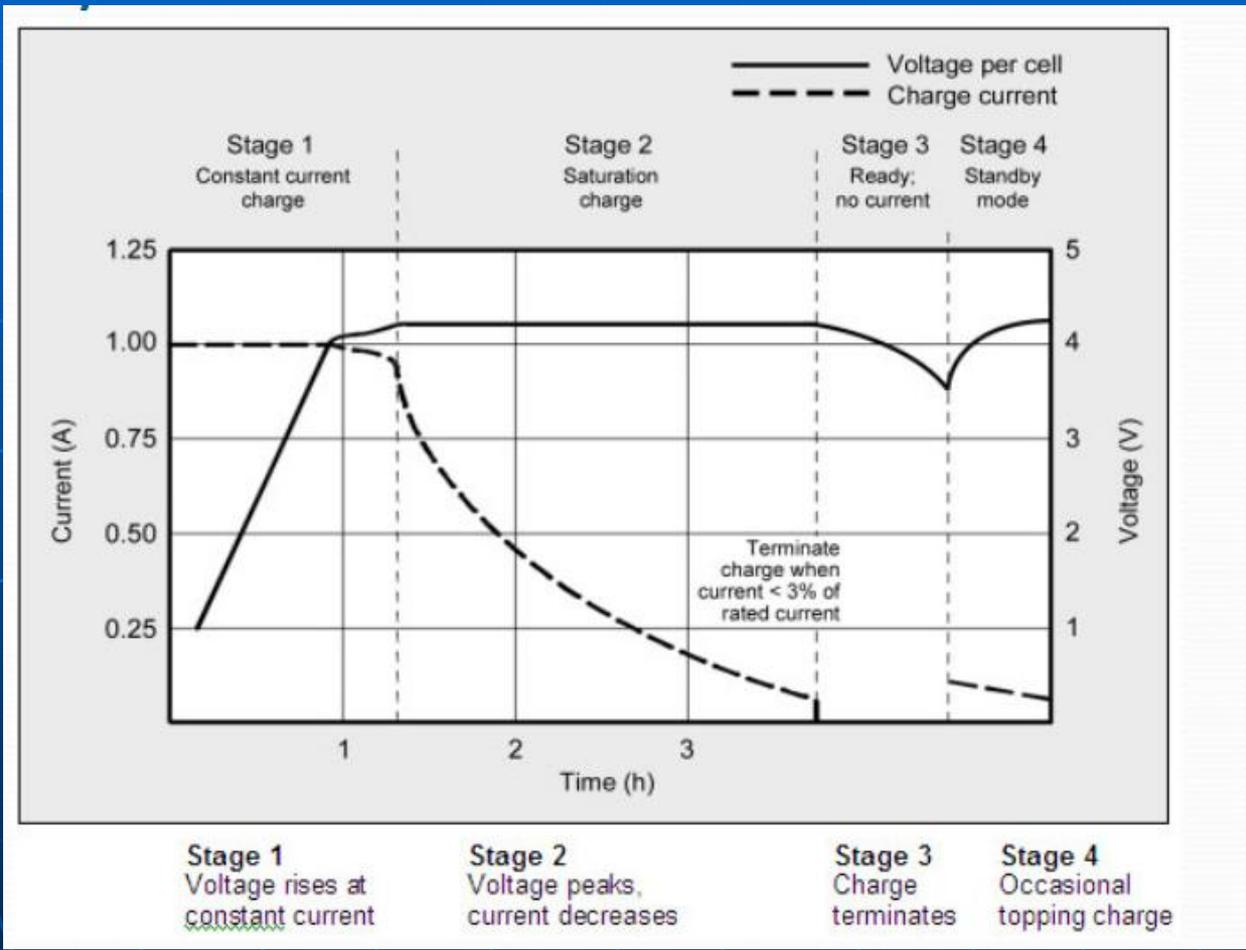


Flow Chart with buck

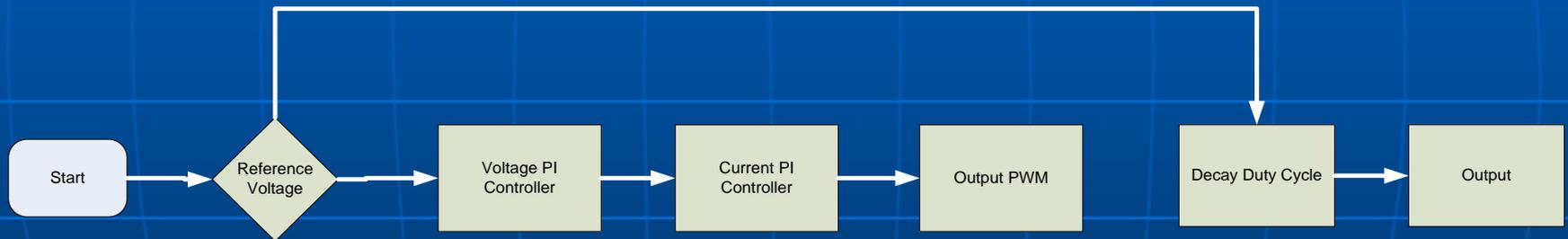


Simulink Model

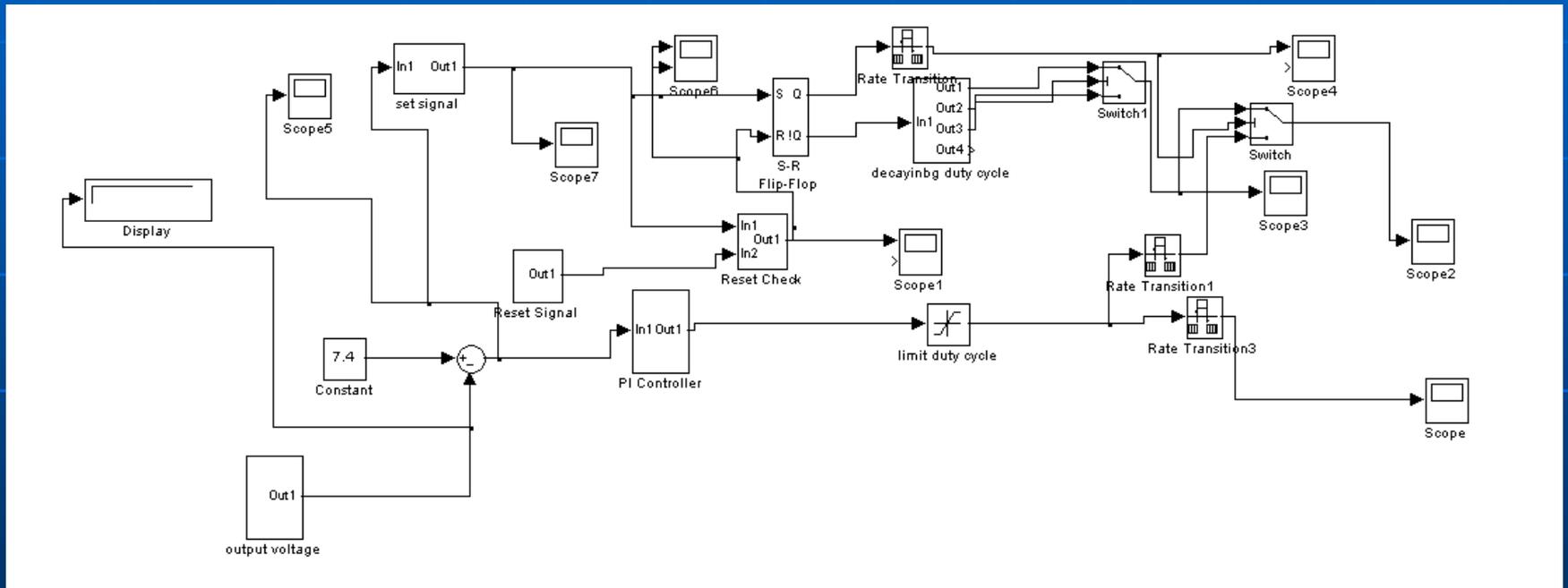


Full Buck System

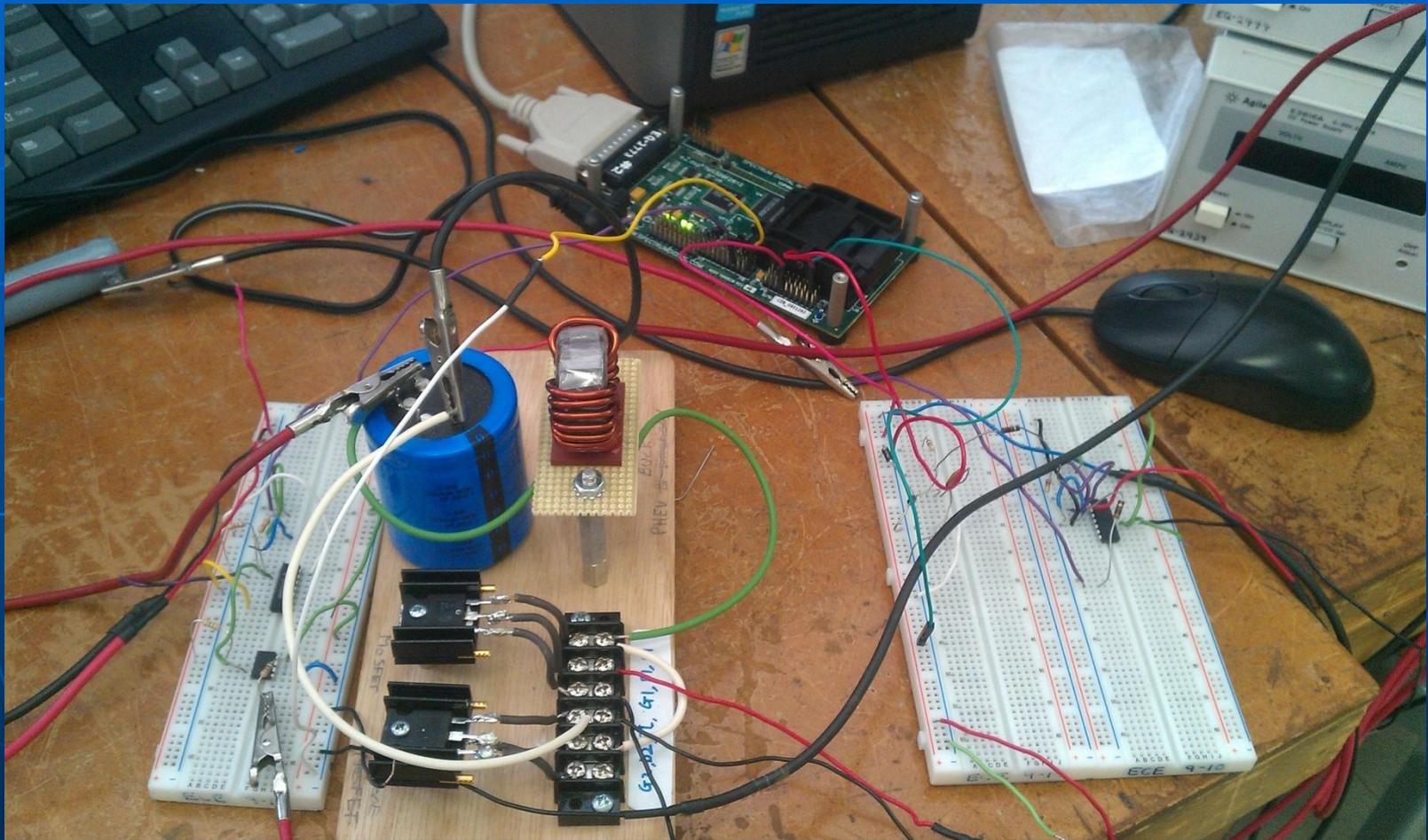

Designing the Voltage Sensing Circuit

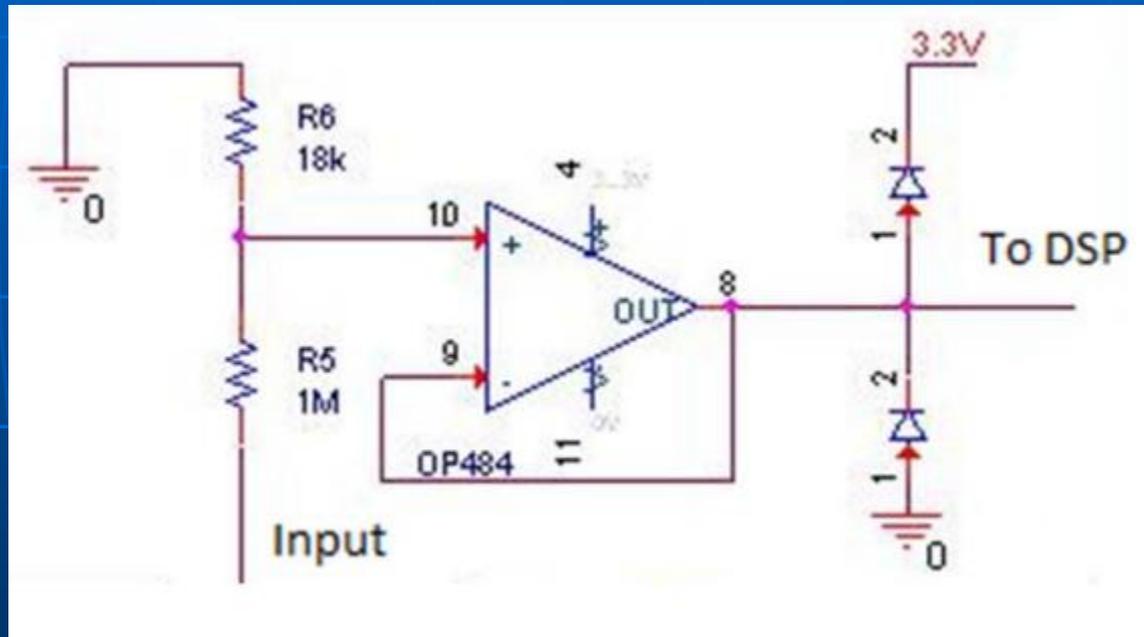

Current Sensor

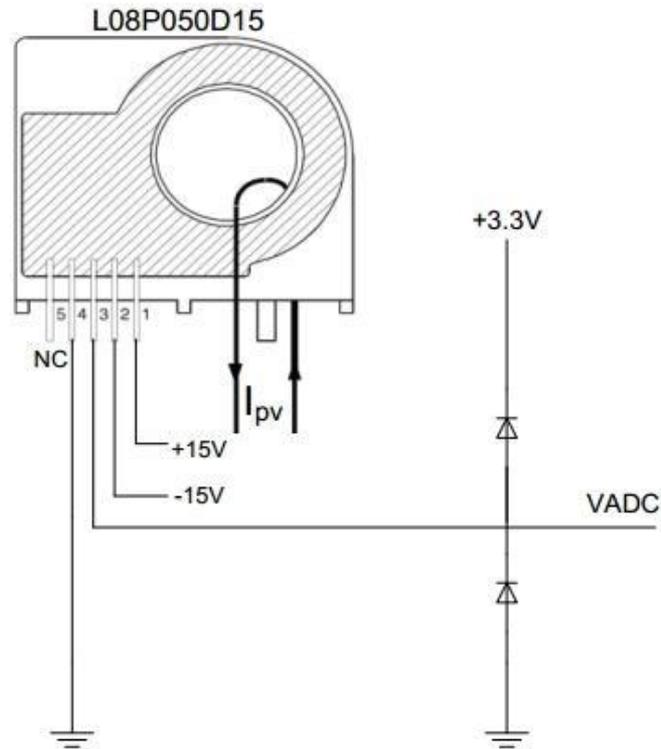

DSP Board Specs

The control algorithm is implemented by a Texas Instruments TMS320F2812 32-bit fixed-point DSP. It has the following features:


- high-performance static CMOS technology, 150 MHz (6.67-ns cycle time);
- high-performance 32-bit CPU;
- Flash devices: up to 128 K × 16 Flash;
- 12-bit ADC, 16 channels.

Why use DSP?


- Fast, reliable, and Ideal for controlling
- Generates a pulse width modulated signal
- Voltage values are calculated by DSP algorithms



Overall System Design

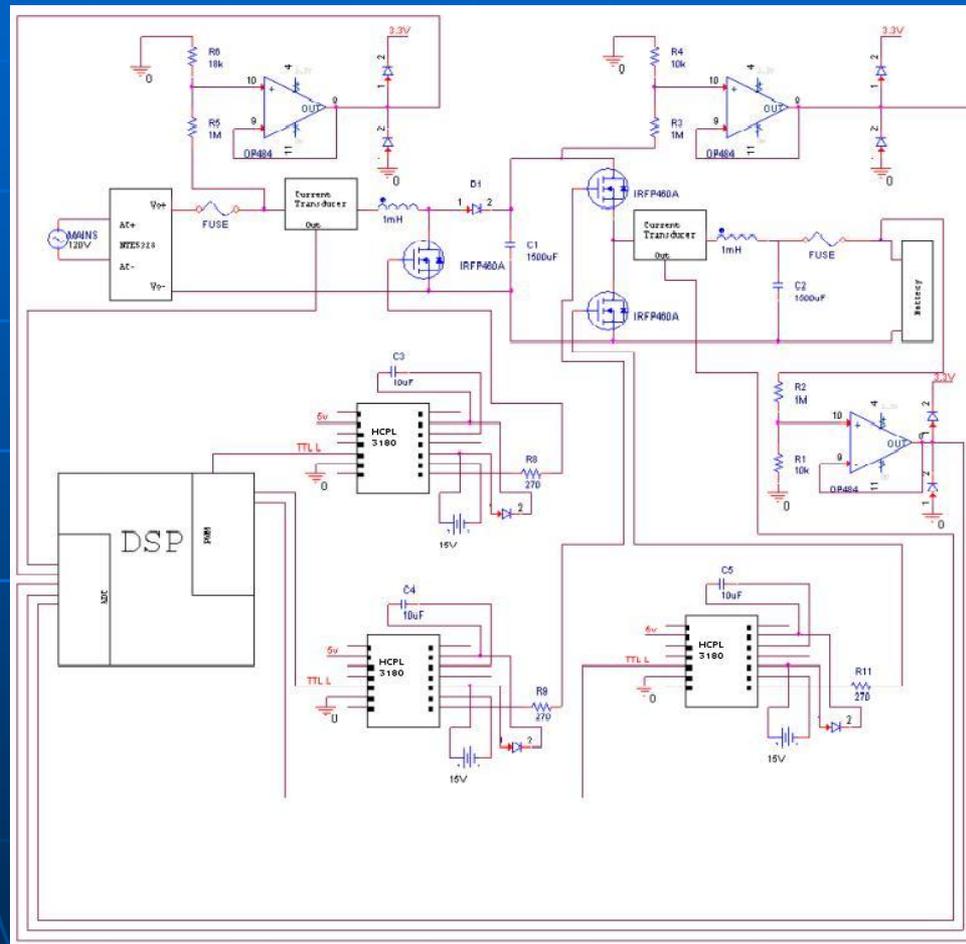

Results

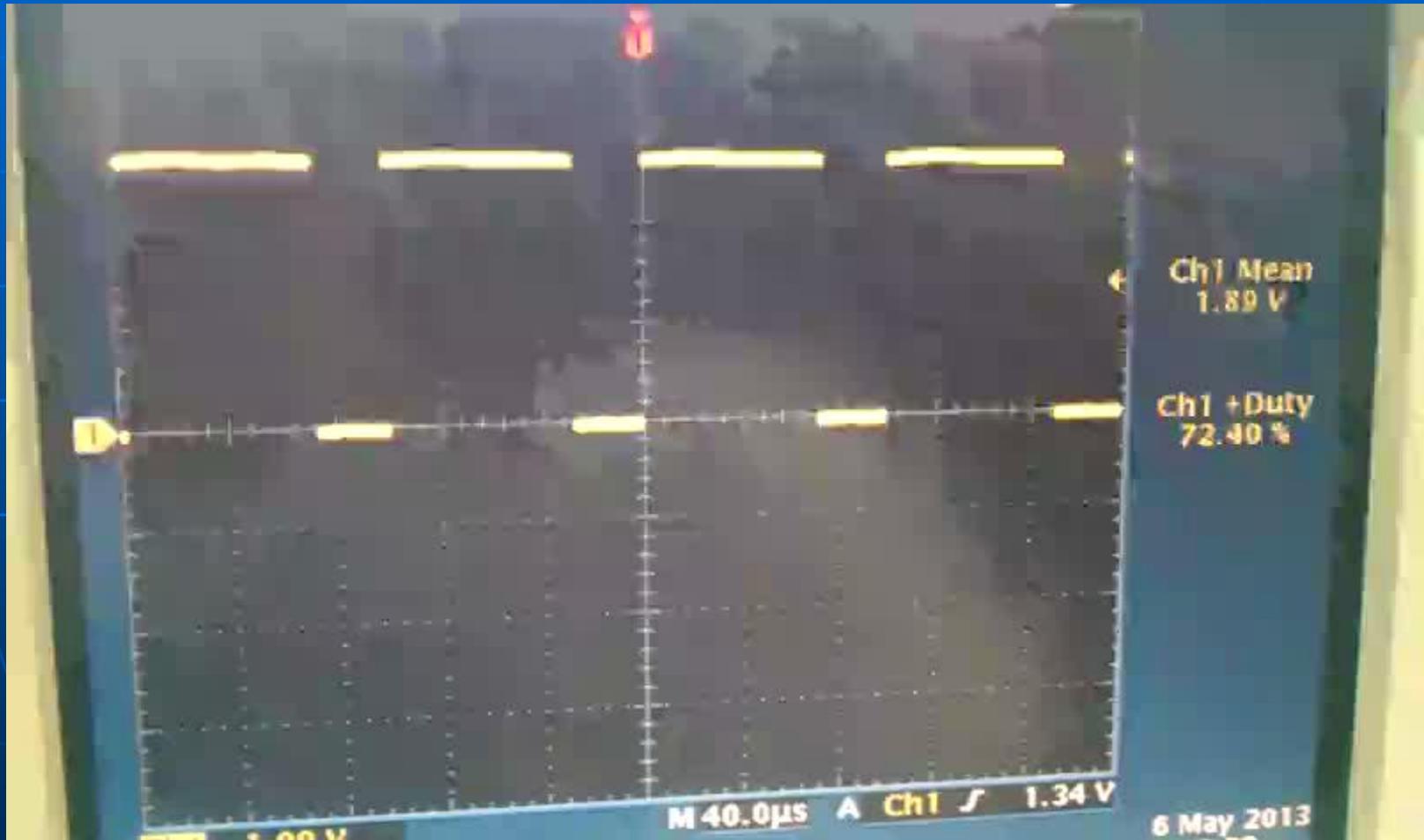

Completed Work

- Battery Testing
- Bi-directional and PFC Redesigned
- Buck Charging model

Future Work

- PCB Designing
- Discharge the battery through an inverter to run a variable load
- Build a protective structure for the battery

References

- [1] N. Mohan. First Course on Power Electronics. Minneapolis: MNPERE, 2009.
- [2] Daly, et. Al. "Electric Vehicle Charger for Plug-In Hybrid Electric Vehicles." PHEV: Plug-in Hybrid Electric Vehicle Charger. 26 Sept. 2011. Web, 24 Sept. 2012.
- [3] B. Bagci. "Programming and use of TMS320F2812 DSP to control and regulate power electronic converters." Master Thesis, Fachhochschule Koln University of Applied Sciences, Cologne, Germany, 2003.
- [4] G. Mathieu, "Design of an on-board charger for plug-in hybrid electrical vehicle (PHEV)," Master Thesis, Chalmers University of Technology, Goteborg, Sweden, 2009.
- [5] L. Zhou, "Evaluation and DSP based implementation of PWM approaches for single-phased DC-AC converters," Master Thesis, Florida State University, Tallahassee, Florida, United States 2005.
- [6] M. Hedlund, "Design and construction of a bidirectional DCDC converter for an EV application," Master Thesis, Uppsala University, Uppsala, Sweden, 2010.
- [7] Y. Tian, "Analysis, simulation and DSP based implementation of asymmetric three-level single phase inverter in solar power system," Master Thesis, Florida State University, Tallahassee, Florida, United States, 2007.
- [8] Application Note AN-978, <http://www.irf.com/technical-info/appnotes/an-978.pdf>
- [9] <http://www.nrel.gov/vehiclesandfuels/energystorage/pdfs/evs17paper2.pdf>
- [10] M. Chen, "Accurate Electrical Battery Model Capable of Predicting Runtime and I-V Performance," IEEE Transaction, Vol. 21, No. 2, June 2006.

Questions?